
CSE477

VLSI Digital Circuits


Fall 2002

Lecture 27: System Level Interconnect

Mary Jane Irwin (www.cse.psu.edu/~mji)
www.cse.psu.edu/~cg477

[Adapted from Rabaey's *Digital Integrated Circuits*, ©2002, J. Rabaey et al.]

Nature of Interconnect

 

Global Interconnect


- ❑ System level signal interconnect - buses
- ❑ Vdd and Gnd planes
- ❑ System clock

Impact of Interconnect Parasitics

- ❑ Reduced reliability
- ❑ Reduced performance

- ❑ Classes of parasitics
 - ❑ capacitive
 - ❑ resistive
 - ❑ inductive



System Level Signal Interconnect

 


- ❑ Many drivers - only one active at a time
- ❑ Many receivers - many may be active at a time

Tristate Buffers

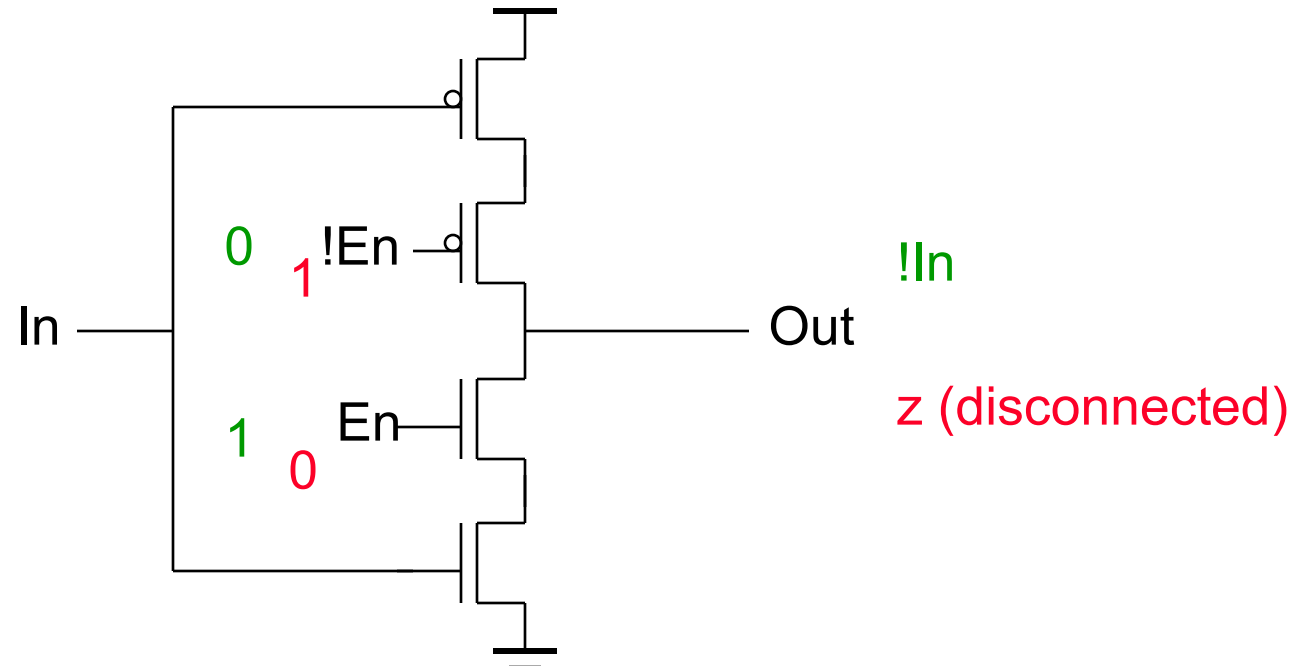 Three states - 0, 1, and z (high impedance)




Reducing Effective Capacitance

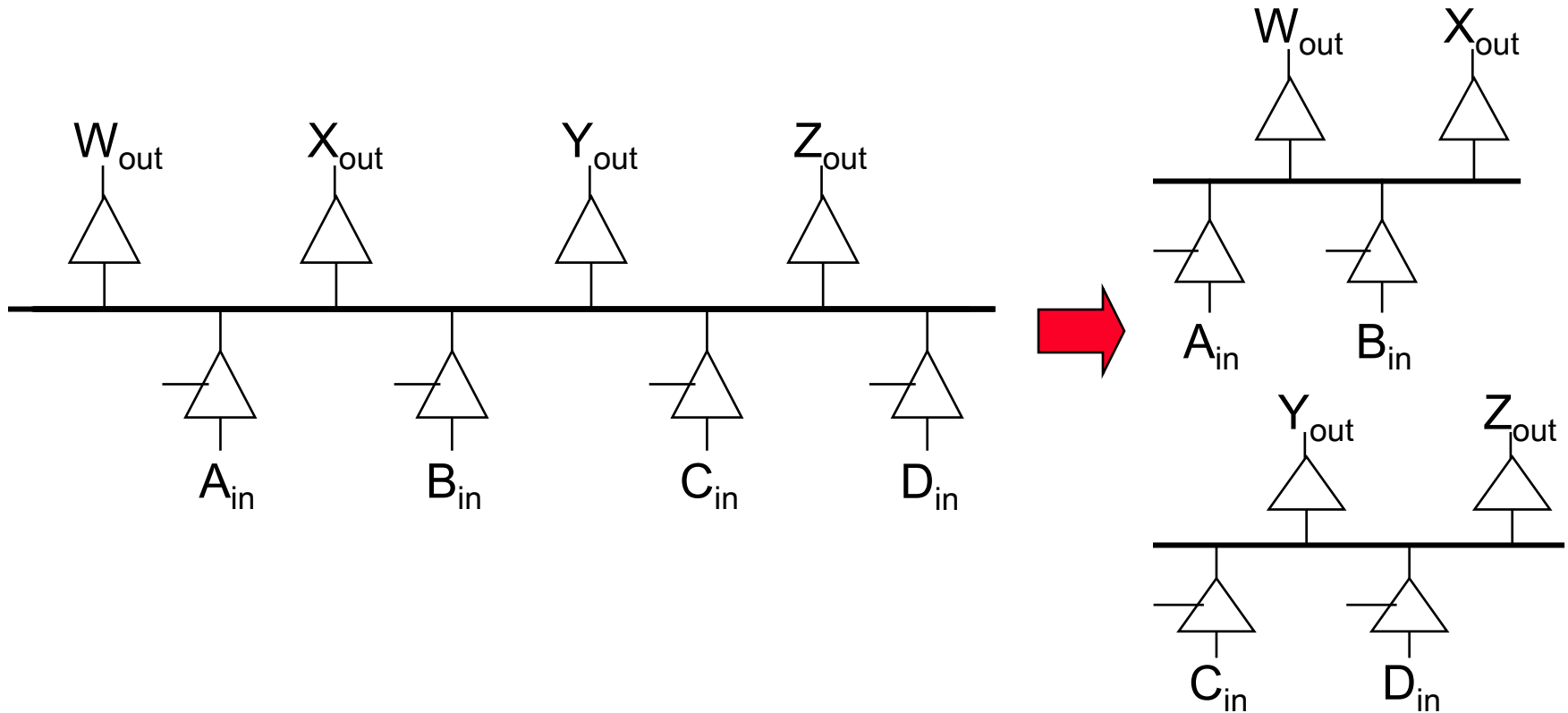

- ❑ Shared resources may also incur extra switching activity


Driving Large Capacitances

 

$$t_{pHL} = \frac{C_L V_{\text{swing}/2}}{I_{\text{av}}}$$

Increase with transistor sizing
 $I_D = k'/2 \ W/L \ (\dots)$

Single Inverter as buffer

 


Total propagation delay = $t_p(\text{inv}) + t_p(\text{buffer})$

t_{p0} - delay of minimum sized inverter with single minimum sized inverter for fanout

$$t_p = u \cdot t_{p0} + x/u \cdot t_{p0}$$


$$u_{\text{opt}} = \sqrt{x}; t_{p,\text{opt}} = 2 \cdot t_{p0} \cdot \sqrt{x}$$

Use Cascaded Buffers

 

$$u_{\text{opt}} = e$$

t_p as a Function of u and x

 

Impact of Cascading Buffers

x	Unbuffered	Single Buffer	Cascaded Buffers
10	10	6.3	6.3
100	100	20	12.5
1,000	1,000	63	18.8
10,000	10,000	200	25


chip bus

I/O pads


t_{opt}/t_{p0} versus x for various driver configurations

$C_{\text{in}} = 10 \text{ fF}$ in 1 micron CMOS

Designing Large Transistors

 

Small transistors in parallel

 


Circular transistors


Capacitive Coupling (Crosstalk)

- ❑ Signal wire glitches as large as 80% of the supply voltage will be common due to crosstalk between neighboring wires as feature sizes continue to scale

Crosstalk vs. Technology

 

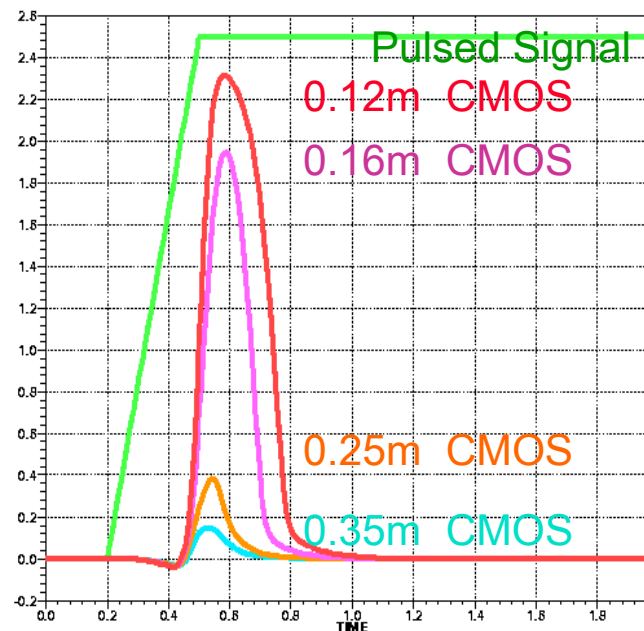Black line quiet —————
Red lines pulsed - - - - -
Glitches strength vs technology




From Dunlop, Lucent, 2000

Battling Capacitive Crosstalk


❑ Avoid parallel lines

❑ Use shielding

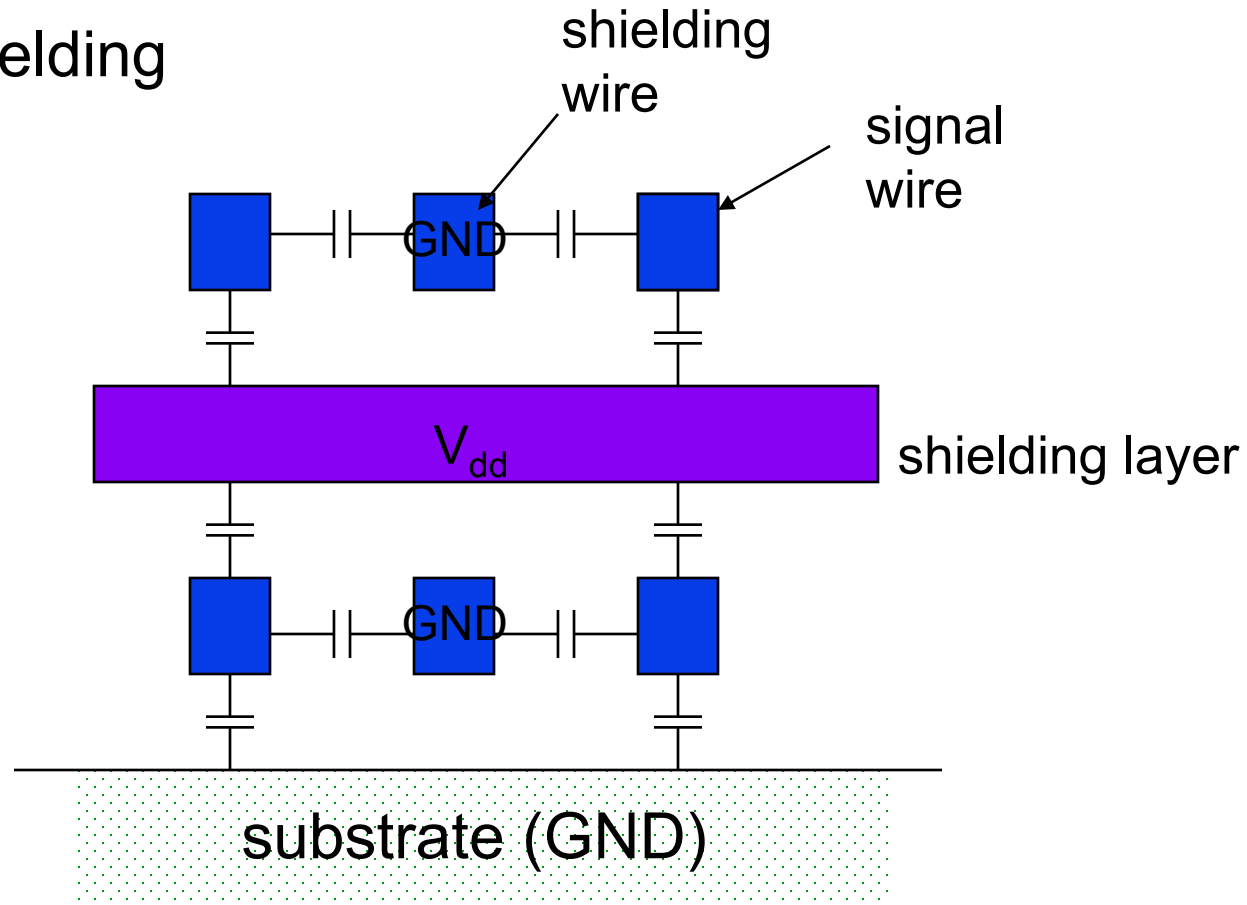

Inductive Effects

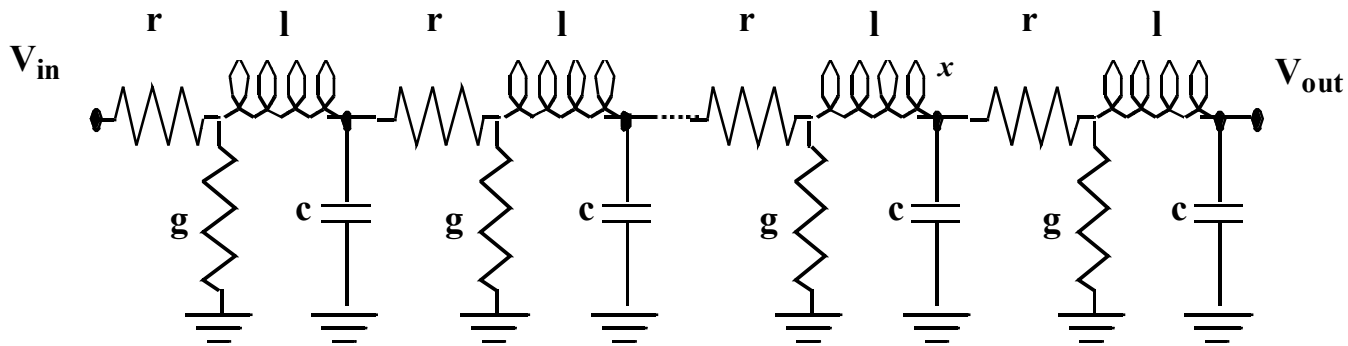- When wires are sufficiently long or circuits are sufficiently fast, **inductance** of the wire starts to dominate the delay behavior



- Must consider wire transmission line effects
 - Wave mode instead of diffusion equations used so far
 - Signal alternately transfers energy from capacitive to inductive modes


Transmission Line Considerations

- ❑ Transmission line effects should be considered when the rise or fall time of the input signal is smaller than the time-of-flight of the transmission line


Rule of Thumb

$$t_r \text{ (} t_f \text{)} < 2.5 t_{\text{flight}} = 2.5 L/v$$

Power and Ground Distribution

 

(a) Finger-shaped network

 

(b) Network with multiple supply pins

Next Lecture and Reminders

□ Next lecture

□ Design for test

- Reading assignment – Rabaey, et al, xx

□ Reminders

□ Project final reports due today

□ Final grading negotiations/correction (except for the final exam) must be concluded by December 10th

□ Final exam scheduled

- Monday, December 16th from 10:10 to noon in 118 and 121 Thomas