
CSE477

VLSI Digital Circuits


Fall 2002

Lecture 07: Pass Transistor Logic

Mary Jane Irwin (www.cse.psu.edu/~mji)
www.cse.psu.edu/~cg477

[Adapted from Rabaey's *Digital Integrated Circuits*, ©2002, J. Rabaey et al.]

Review: Static Complementary CMOS

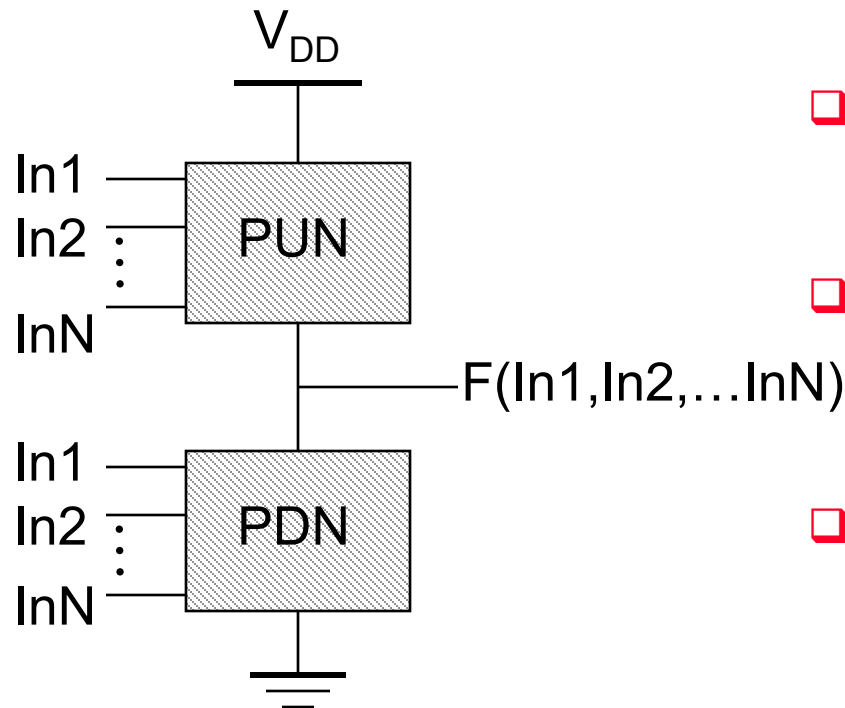


PUN and PDN are **dual** logic networks

- ❑ High noise margins
 - ❑ V_{OH} and V_{OL} are at V_{DD} and GND, respectively
- ❑ Low output impedance, high input impedance
- ❑ No static power consumption
 - ❑ Never a direct path between V_{DD} and GND in steady state
- ❑ Delay a function of load capacitance and transistor on resistance
- ❑ Comparable rise and fall times (under the appropriate relative transistor sizing conditions)

Review: Static CMOS Full Adder Circuit

$$\neg C_{out} = \neg C_{in} (\neg A \vee \neg B) \vee \neg A \neg B$$
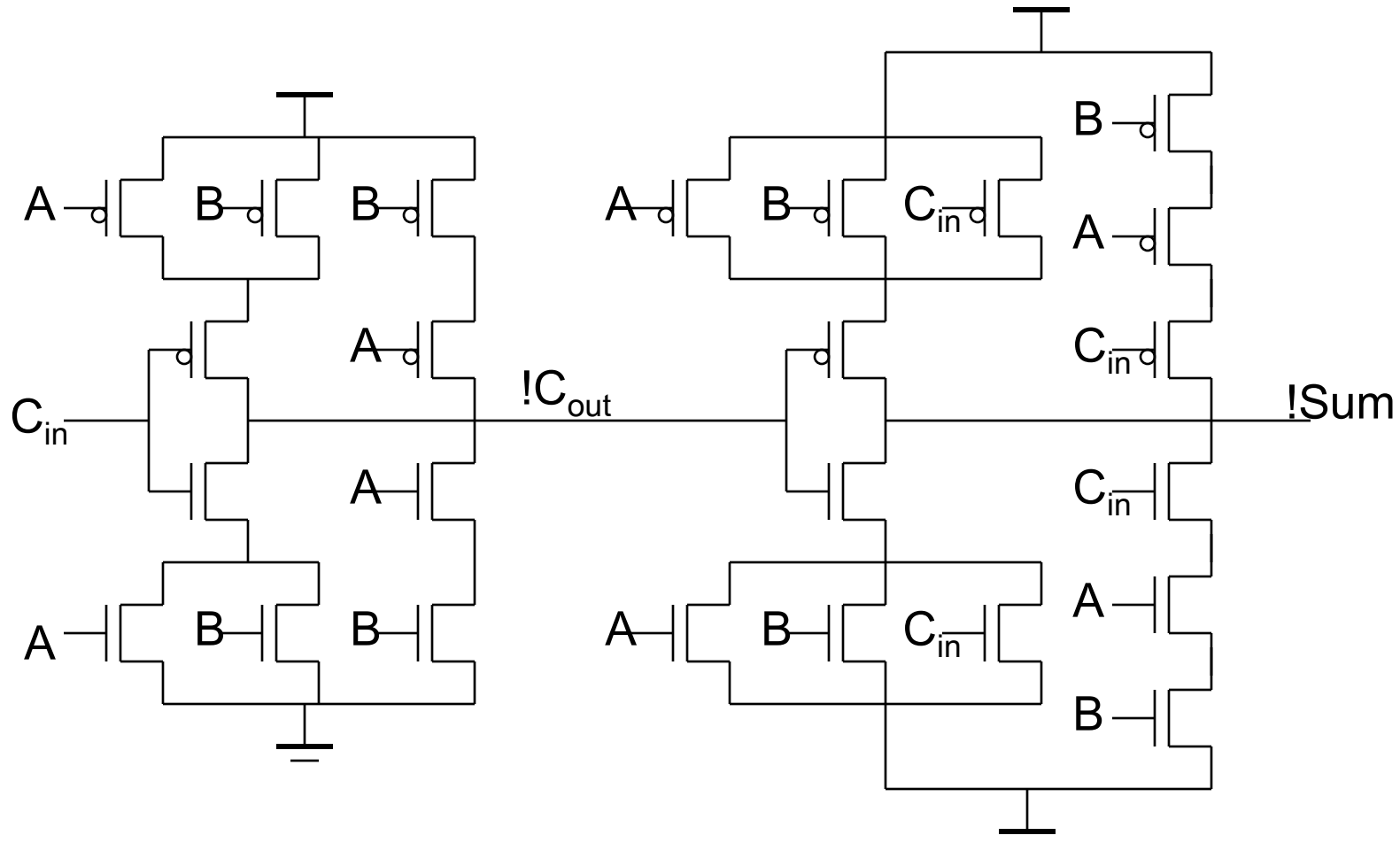
$$\neg Sum = C_{out} (\neg A \vee \neg B \vee \neg C_{in}) \vee \neg A \neg B \neg C_{in}$$




$$C_{out} = C_{in} (A \vee B) \vee A B$$


$$Sum = \neg C_{out} (A \vee B \vee C_{in}) \vee A B C_{in}$$

NMOS Transistors in Series/Parallel

 - ❑ Primary inputs drive both gate and source/drain terminals
- ❑ NMOS switch closes when the gate input is high



$X = Y$ if A and B

 


$X = Y$ if A or B


- ❑ Remember - NMOS transistors pass a **strong** 0 but a **weak** 1

PMOS Transistors in Series/Parallel

 - ❑ Primary inputs drive both gate and source/drain terminals
- ❑ PMOS switch closes when the gate input is low




 
$$X = Y \text{ if } \overline{A} \text{ and } \overline{B} = \overline{A + B}$$



$$X = Y \text{ if } \overline{A} \text{ or } \overline{B} = \overline{A \bullet B}$$



- ❑ Remember - PMOS transistors pass a **strong** 1 but a **weak** 0

Pass Transistor (PT) Logic

  






- ❑ Gate is static – a low-impedance path exists to both supply rails under all circumstances
- ❑ N transistors instead of 2N
- ❑ No static power consumption
- ❑ Ratioless
- ❑ Bidirectional (versus unidirectional)

VTC of PT AND Gate

  

- Pure PT logic is not **regenerative** - the signal gradually degrades after passing through a number of PTs (can fix with static CMOS inverter insertion)


Differential PT Logic (CPL)

     


CPL Properties

- ❑ **Differential** so complementary data inputs and outputs are always available (so don't need extra inverters)
- ❑ Still static, since the output defining nodes are always tied to V_{DD} or GND through a low resistance path
- ❑ Design is **modular**; all gates use the same topology, only the inputs are permuted.
- ❑ Simple XOR makes it attractive for structures like **adders**
- ❑ Fast (assuming number of transistors in series is small)
- ❑ Additional routing overhead for complementary signals
- ❑ Still have static power dissipation problems

CPL Full Adder

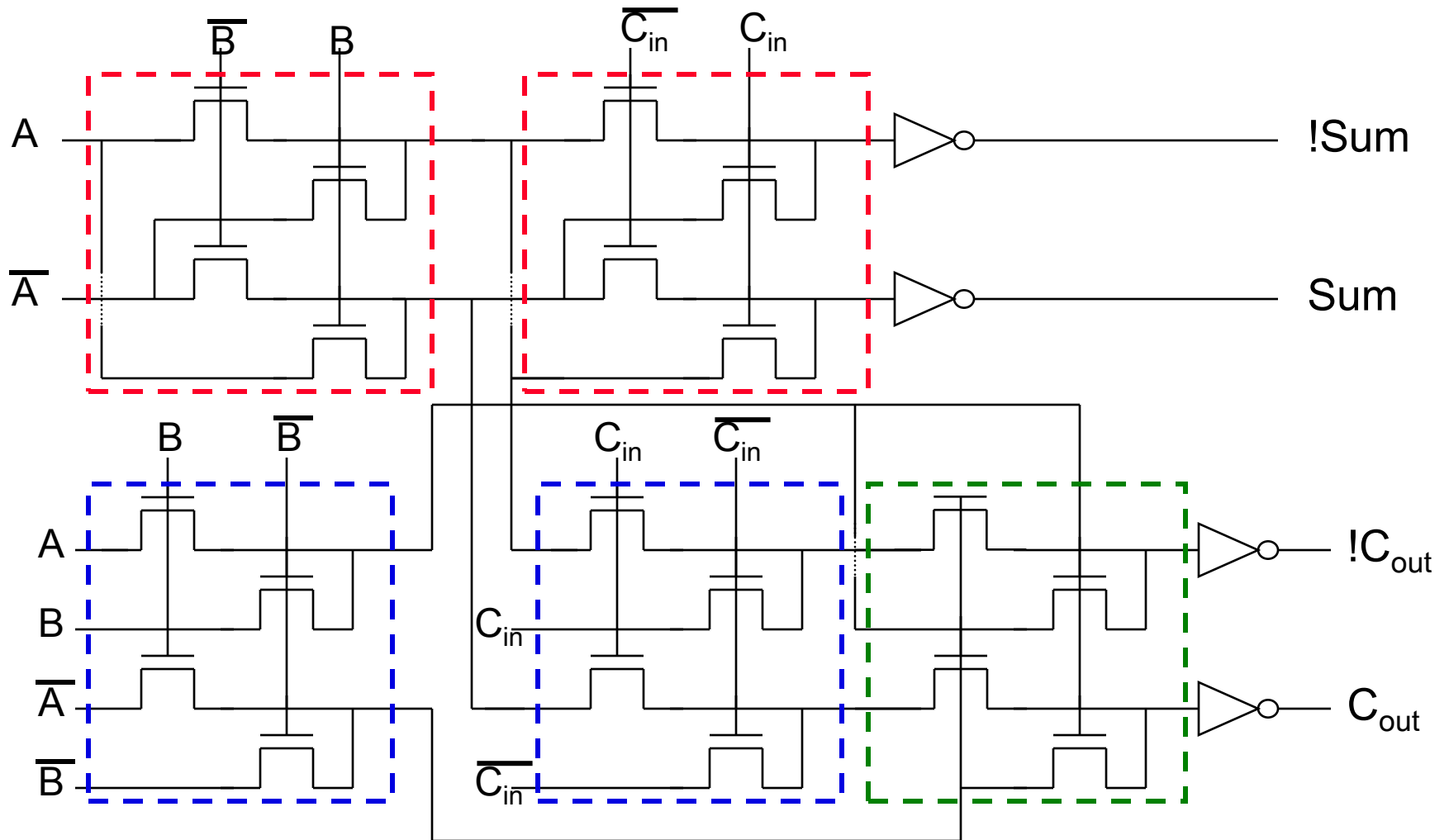


NMOS Only PT Driving an Inverter

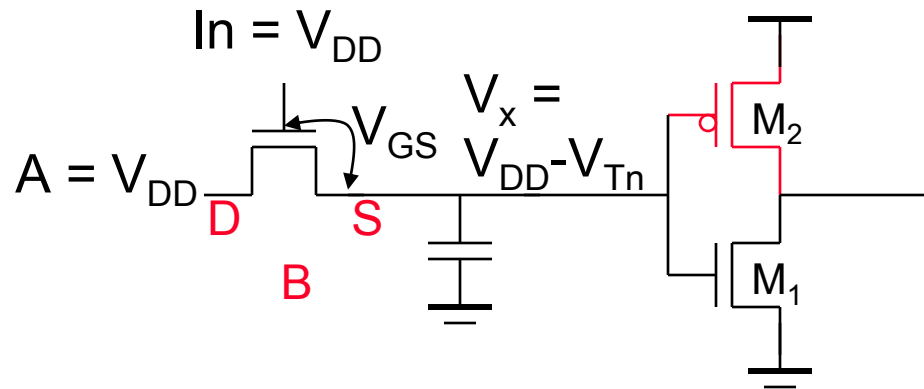

- ❑ V_x does not pull up to V_{DD} , but $V_{DD} - V_{Tn}$
- ❑ Threshold voltage drop causes static power consumption (M_2 may be weakly conducting forming a path from V_{DD} to GND)
- ❑ Notice V_{Tn} increases of pass transistor due to **body effect** (V_{SB})


Voltage Swing of PT Driving an Inverter

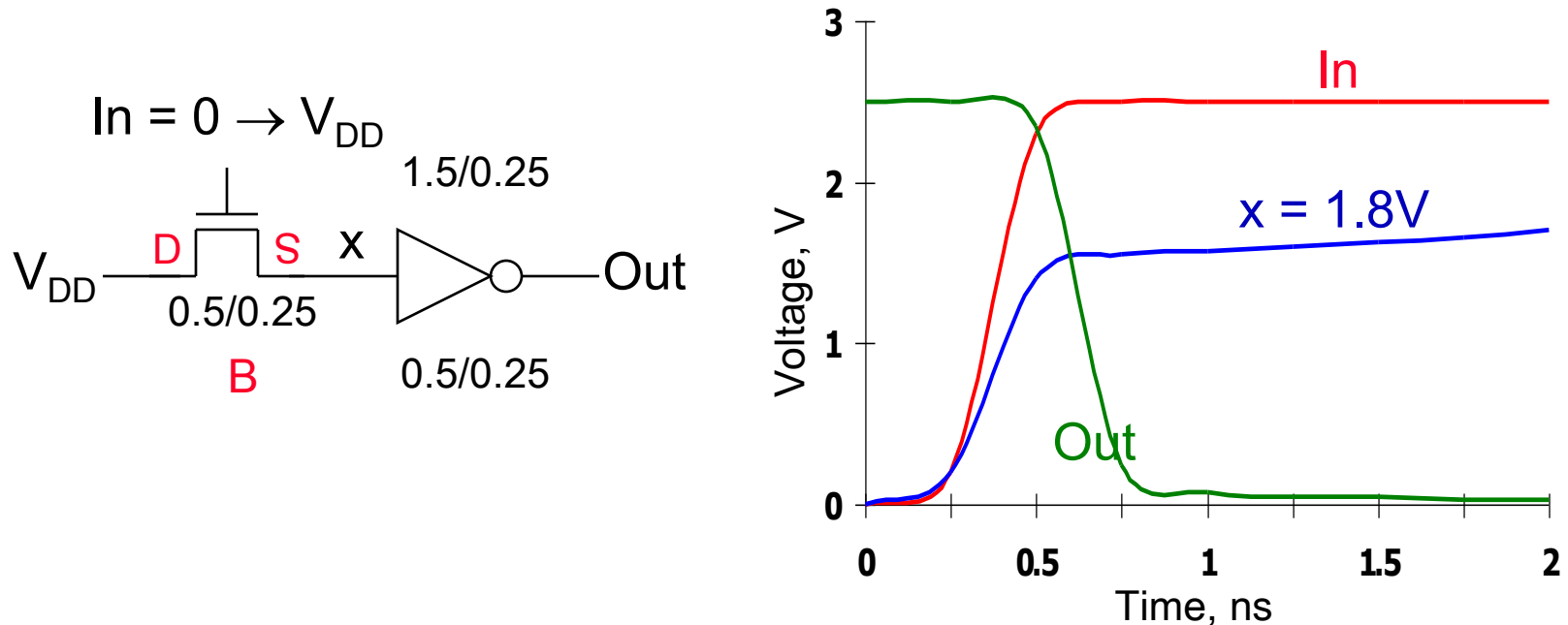

- ❑ **Body effect** – large V_{SB} at x - when pulling high (B is tied to GND and S charged up close to V_{DD})
- ❑ So the voltage drop is even worse

$$V_x = V_{DD} - (V_{Tn0} + \gamma(\sqrt{(|2\phi_f| + V_x)} - \sqrt{|2\phi_f|}))$$


Cascaded NMOS Only PTs

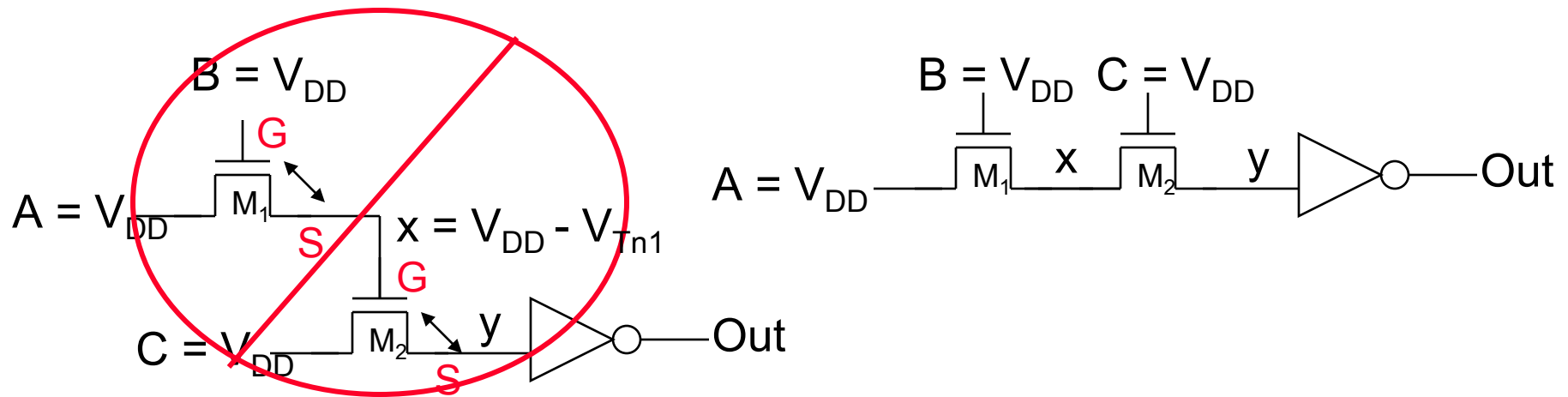

Swing on $y = V_{DD} - V_{Tn1} - V_{Tn2}$


Swing on $y = V_{DD} - V_{Tn1}$

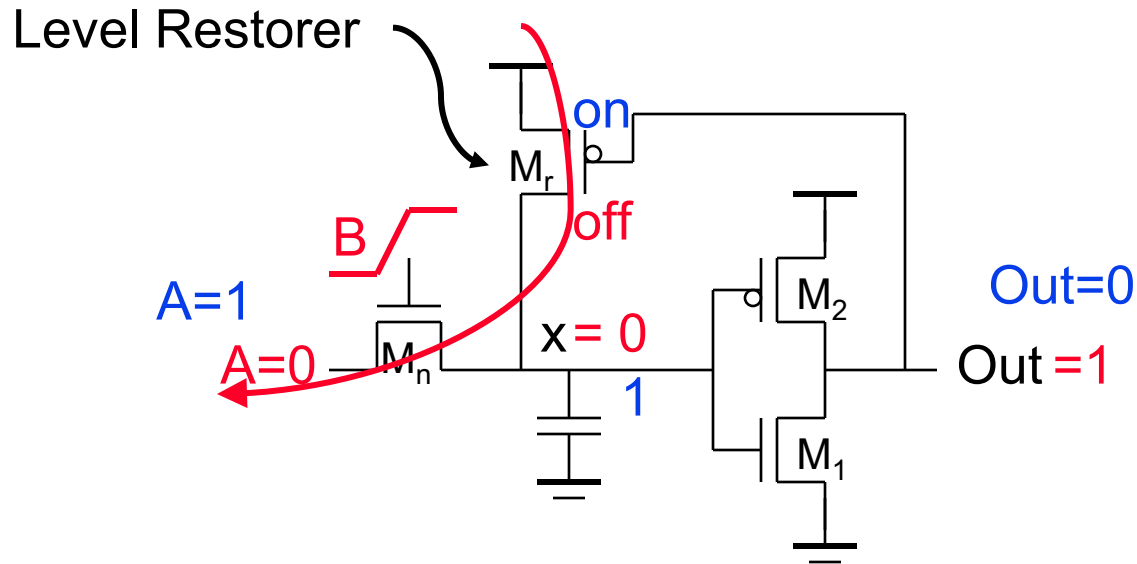- ❑ Pass transistor gates should **never** be cascaded as on the left
- ❑ Logic on the right suffers from static power dissipation and reduced noise margins



- ❑ Full swing on x (due to Level Restorer) so no static power consumption by inverter
- ❑ No static backward current path through Level Restorer and PT since Restorer is only active when A is high
- ❑ For correct operation M_r must be sized correctly (ratioed)

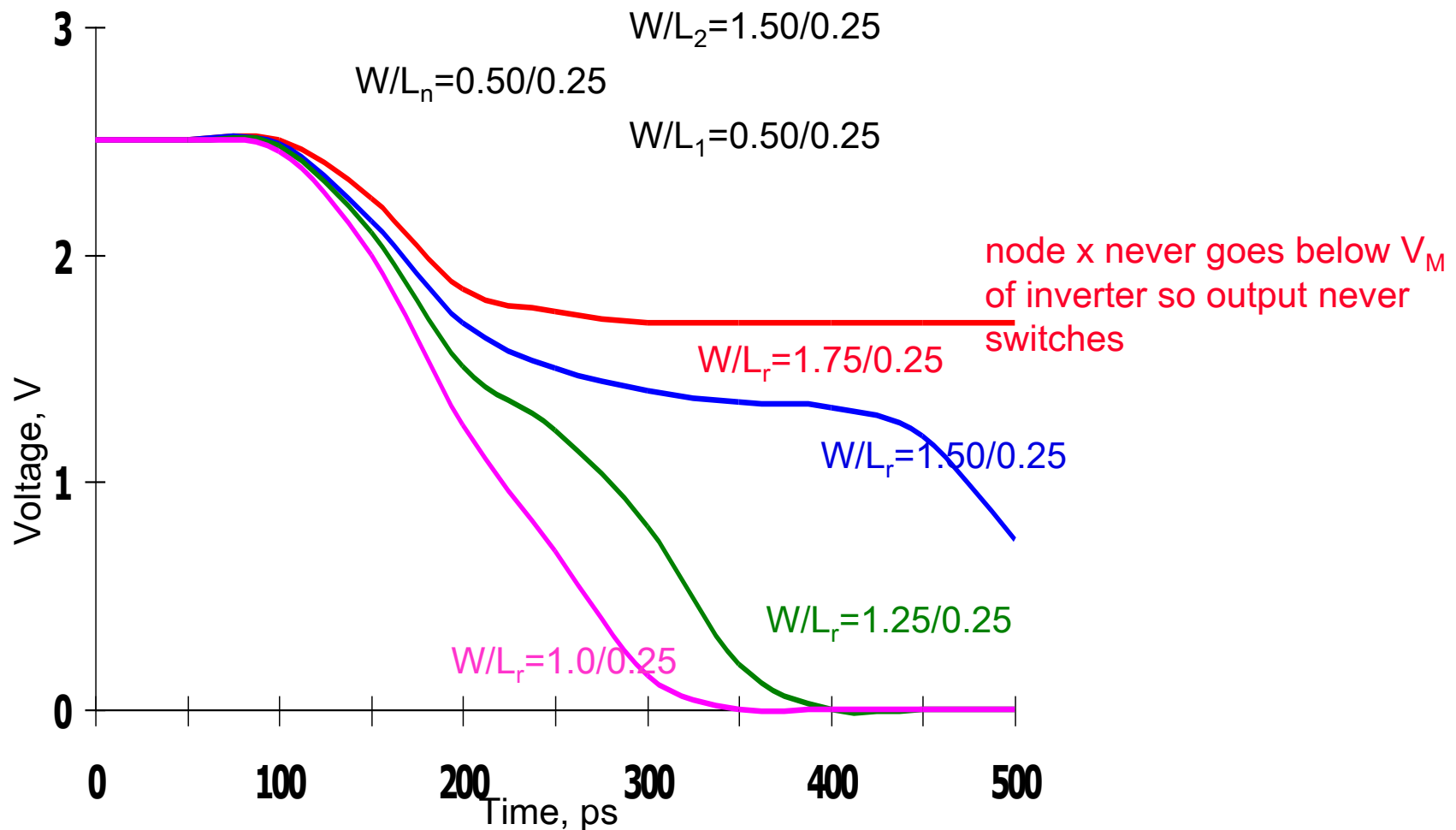
Transient Level Restorer Circuit Response



- ❑ Restorer has speed and power impacts: increases the capacitance at x, slowing down the gate; increases t_r (but decreases t_f)

Solution 2: Multiple V_T Transistors




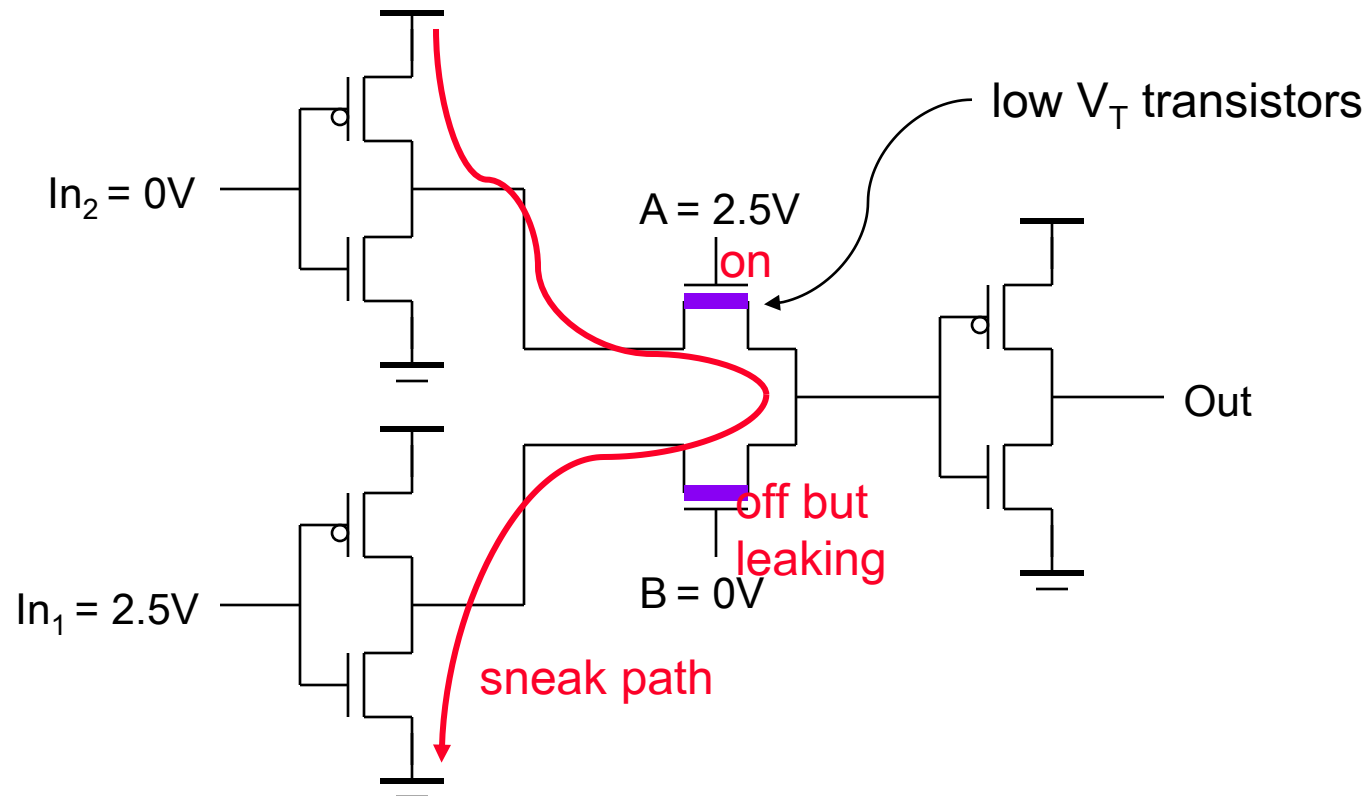
- Technology solution: Use (near) zero V_T devices for the NMOS PTs to eliminate *most* of the threshold drop (body effect still in force preventing full swing to V_{DD})



- Impacts static power consumption due to subthreshold currents flowing through the PTs (even if V_{GS} is below V_T)


Solution 3: Transmission Gates (TGs)

- Most widely used solution

 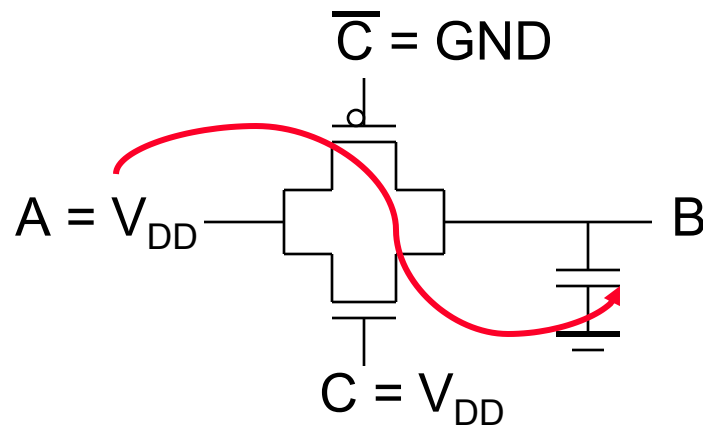  


- Full swing** *bidirectional* switch controlled by the gate signal C, $A = B$ if $C = 1$


Resistance of TG

 


TG Multiplexer

 

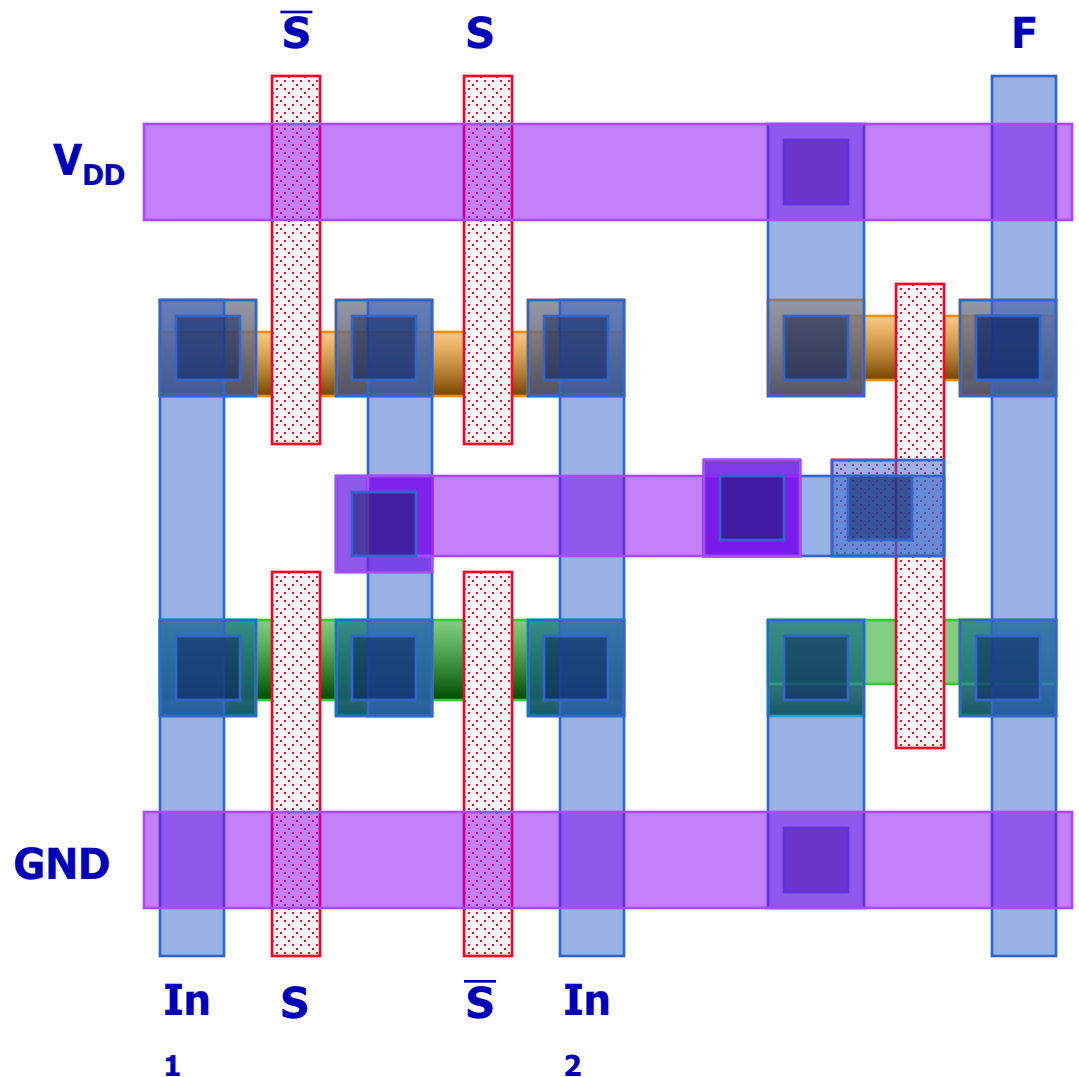
$$F = \neg(In_1 \bullet S + In_2 \bullet \bar{S})$$





Transmission Gate XOR

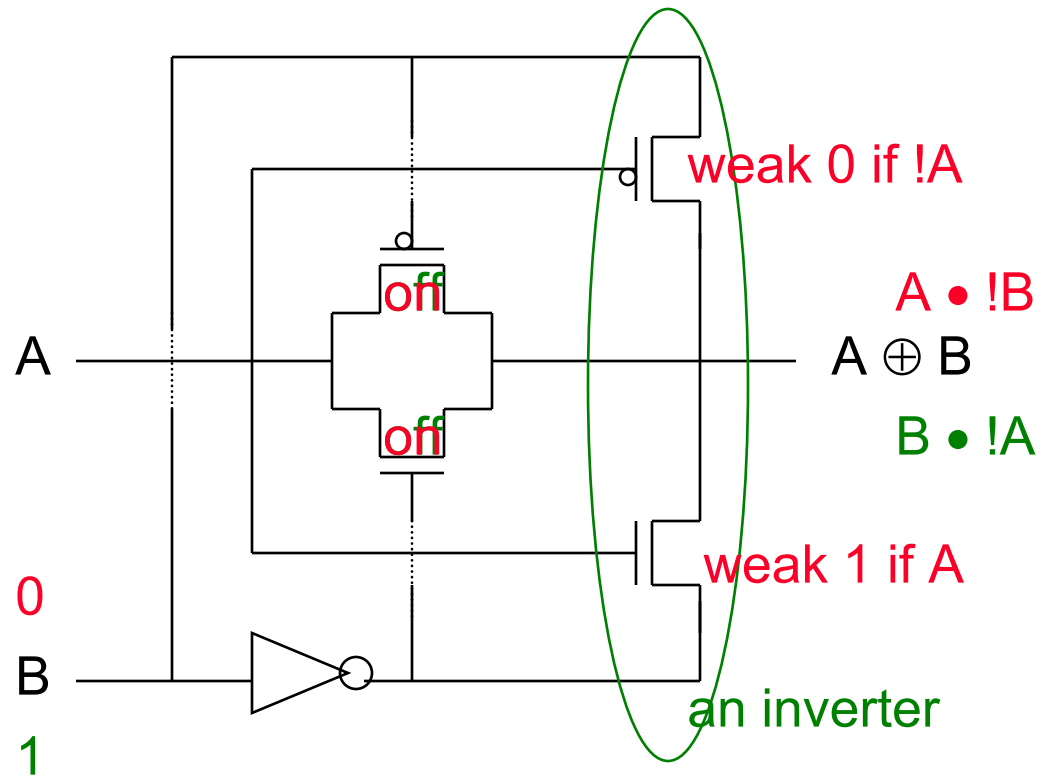

TG Full Adder

 

Differential TG Logic (DPL)

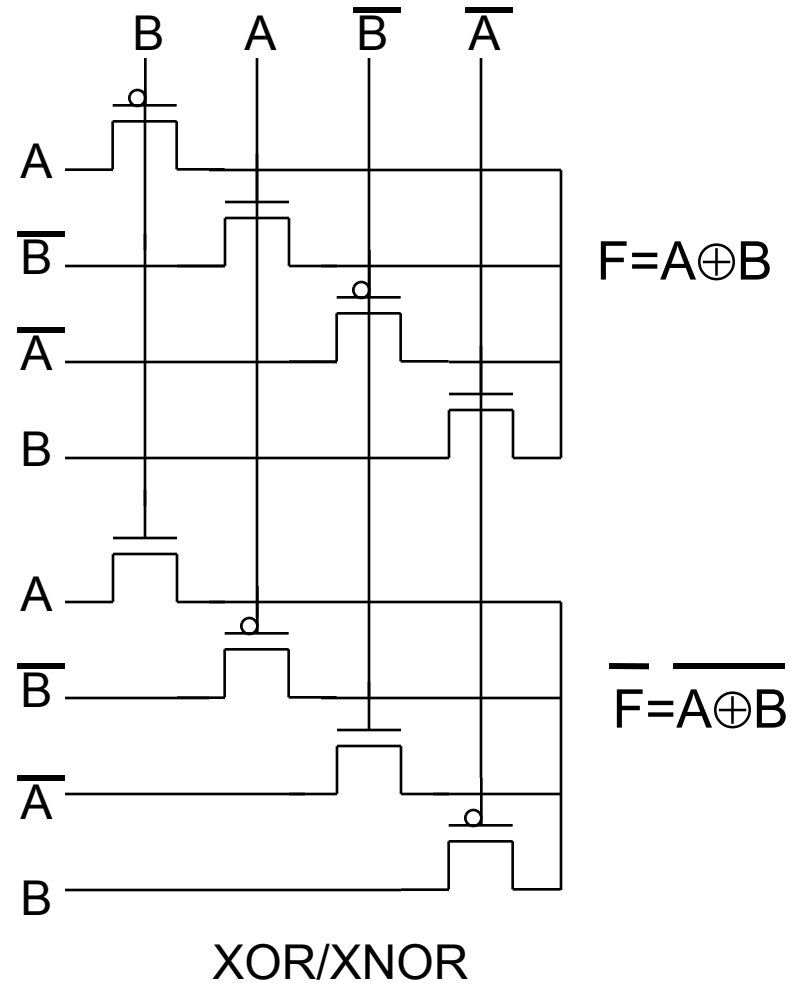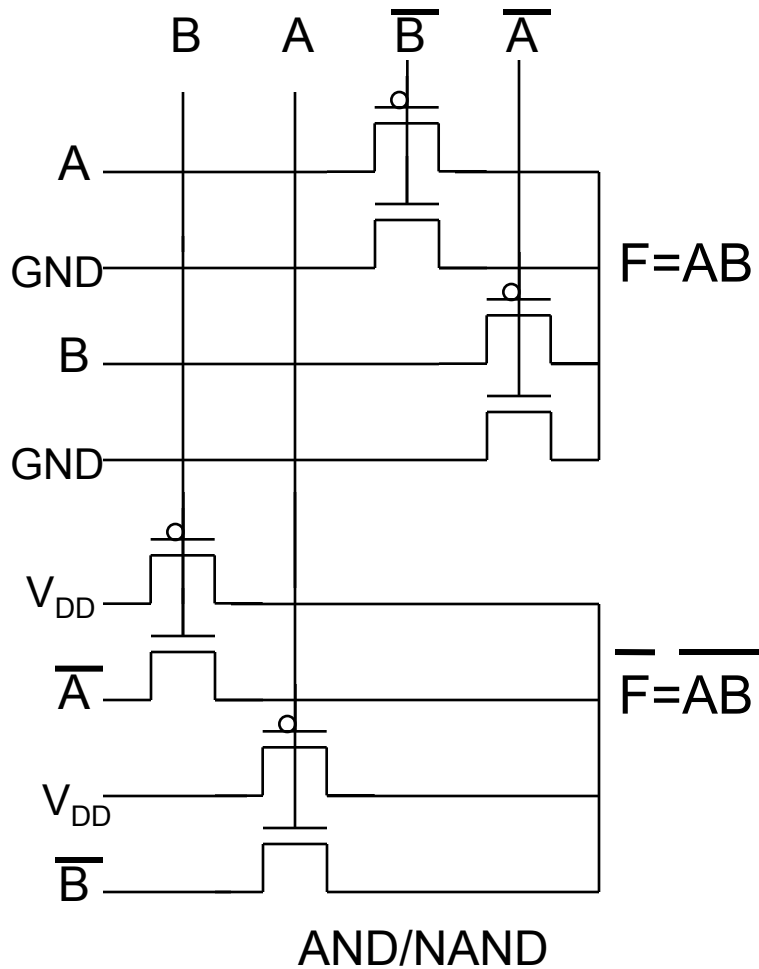

Next Time: The MOS Transistor

- ❑ MOS transistor dynamic behavior (R and C)
- ❑ Wire capacitance

Next Lecture and Reminders

❑ Next lecture

- ❑ MOS transistor dynamic behavior
 - Reading assignment – Rabaey, et al, 3.2.3 & 3.3.3-3.3.5
- ❑ Wiring capacitance
 - Reading assignment – Rabaey, et al, 4.1-4.3.1

❑ Reminders

- ❑ Lecture 5! will be Thursday (guest lecturer)
- ❑ Lecture 8 will be on the 24th and lectures 9+10 will be on the 26th
- ❑ HW2 due September 24th; HW3 handed out then (due Oct 10th)
- ❑ Evening midterm exam scheduled
 - Wednesday, October 16th from 8:15 to 10:15pm in 260 Willard
 - Only one midterm conflict filed for so far