

---

# **CSE477**

## **VLSI Digital Circuits**

### **Fall 2002**

## **Lecture 24: RAM Cores**

Mary Jane Irwin ( [www.cse.psu.edu/~mji](http://www.cse.psu.edu/~mji) )  
[www.cse.psu.edu/~cg477](http://www.cse.psu.edu/~cg477)

[Adapted from Rabaey's *Digital Integrated Circuits*, ©2002, J. Rabaey et al.]

# Review: Basic Building Blocks

---

## ❑ Datapath

### ❑ Execution units

- Adder, multiplier, divider, shifter, etc.

### ❑ Register file and pipeline registers

### ❑ Multiplexers, decoders

## ❑ Control

### ❑ Finite state machines (PLA, ROM, random logic)

## ❑ Interconnect

### ❑ Switches, arbiters, buses

## ❑ Memory

### ❑ Caches (SRAMs), TLBs, DRAMs, buffers

# Review: Read-Write Memories (RAMs)


## ❑ Static – SRAM

- ❑ data is stored as long as supply is applied
- ❑ large cells (6 fets/cell) – so fewer bits/chip
- ❑ fast – so used where speed is important (e.g., caches)
- ❑ differential outputs (output BL and !BL)
- ❑ use sense amps for performance
- ❑ compatible with CMOS technology


## ❑ Dynamic – DRAM

- ❑ periodic refresh required
- ❑ small cells (1 to 3 fets/cell) – so more bits/chip
- ❑ slower – so used for main memories
- ❑ single ended output (output BL only)
- ❑ need sense amps for correct operation
- ❑ not typically compatible with CMOS technology


# Review: 4x4 SRAM Memory

 

# 6-transistor SRAM Cell

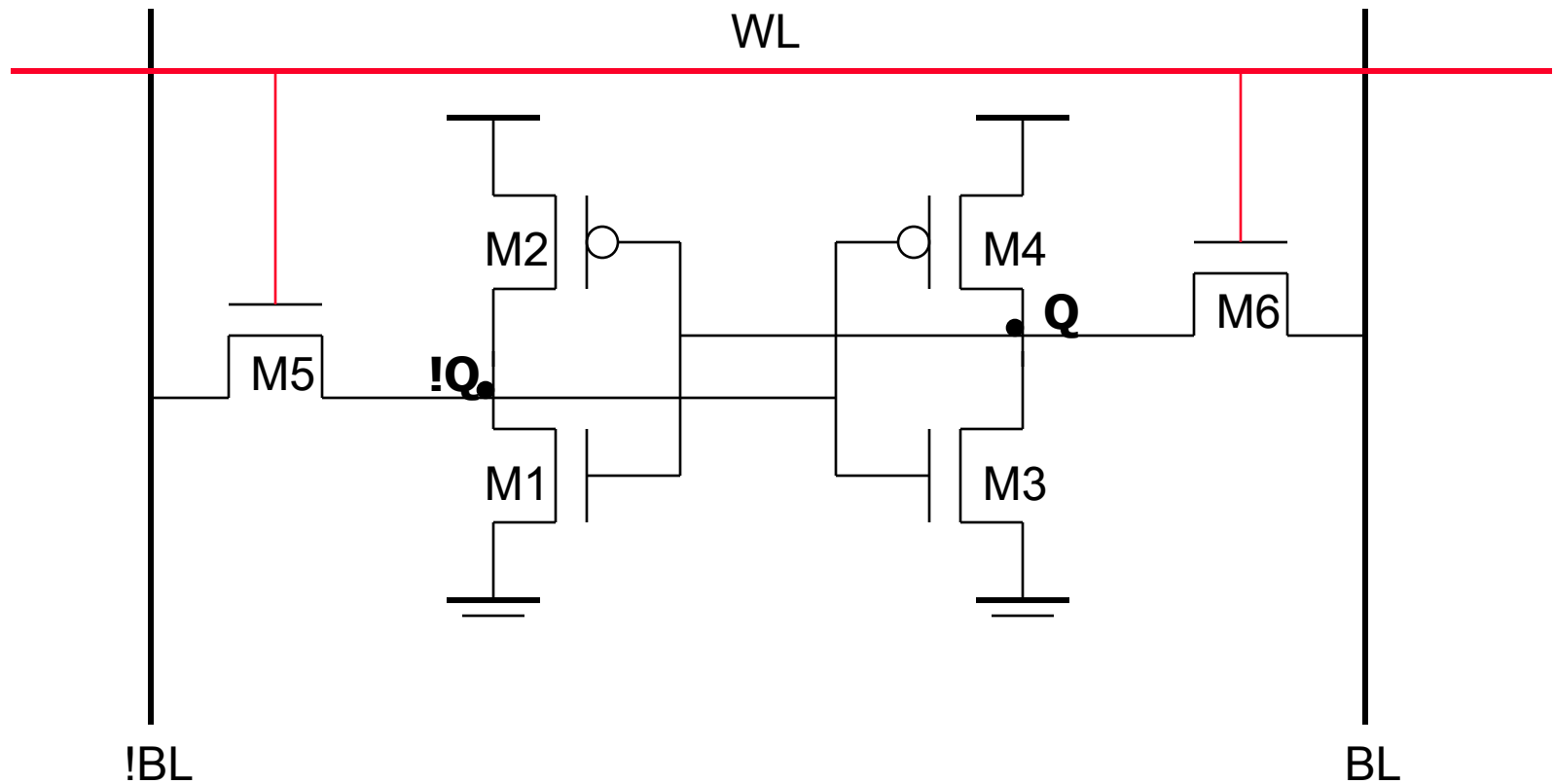


# SRAM Cell Analysis (Read)

 

**Read-disturb (read-upset):** must carefully limit the allowed voltage rise on  $!Q$  to a value that prevents the read-upset condition from occurring while simultaneously maintaining acceptable circuit speed and area constraints

# SRAM Cell Analysis (Read)

 


$$\text{Cell Ratio (CR)} = (W_{M1}/L_{M1})/(W_{M5}/L_{M5})$$

$$V_{!Q} = [(V_{dd} - V_{Tn})(1 + CR \pm \sqrt{CR(1 + CR)})]/(1 + CR)$$


# Read Voltages Ratios

$$V_{dd} = 2.5V$$
$$V_{Tn} = 0.5V$$

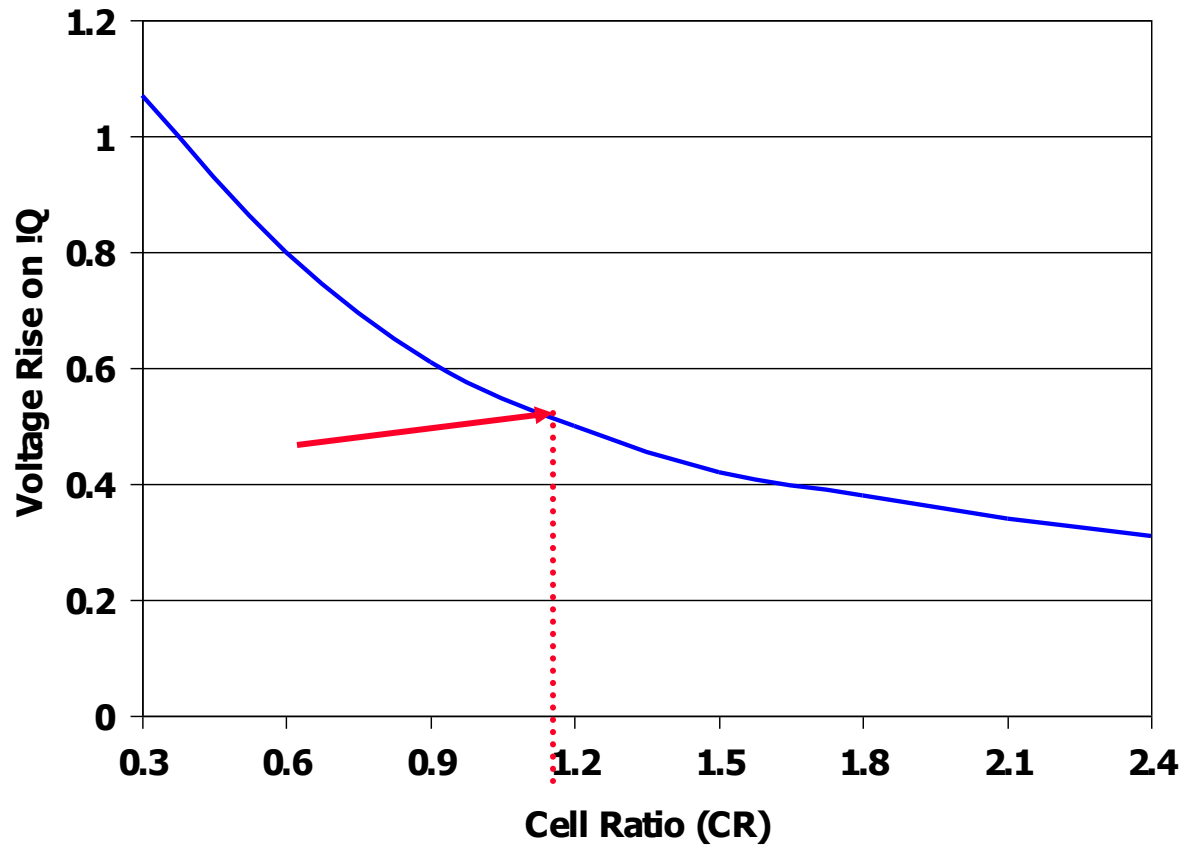



# SRAM Cell Analysis (Write)

 


$$\text{Pullup Ratio (PR)} = (W_{M4}/L_{M4})/(W_{M6}/L_{M6})$$

$$V_Q = (V_{dd} - V_{Tn}) \pm \sqrt{((V_{dd} - V_{Tn})^2 - (\mu_p/\mu_n)(PR)((V_{dd} - V_{Tn} - V_{Tp})^2)}$$

# Write Voltages Ratios

$$V_{dd} = 2.5V$$
$$|V_{Tp}| = 0.5V$$
$$\mu_p/\mu_n = 0.5$$

 


# Cell Sizing


---

- ❑ Keeping cell size minimized is critical for large caches
- ❑ Minimum sized pull down fets (M1 and M3)
  - ❑ Requires minimum width and longer than minimum channel length pass transistors (M5 and M6) to ensure proper CR
  - ❑ But sizing of the pass transistors increases capacitive load on the word lines *and* limits the current discharged on the bit lines both of which can adversely affect the speed of the read cycle
- ❑ Minimum width and length pass transistors
  - ❑ Boost the width of the pull downs (M1 and M3)
  - ❑ Reduces the loading on the word lines and increases the storage capacitance in the cell – both are good! – but cell size may be slightly larger


# 6T-SRAM Layout

 



# Multiple Read/Write Port Cell

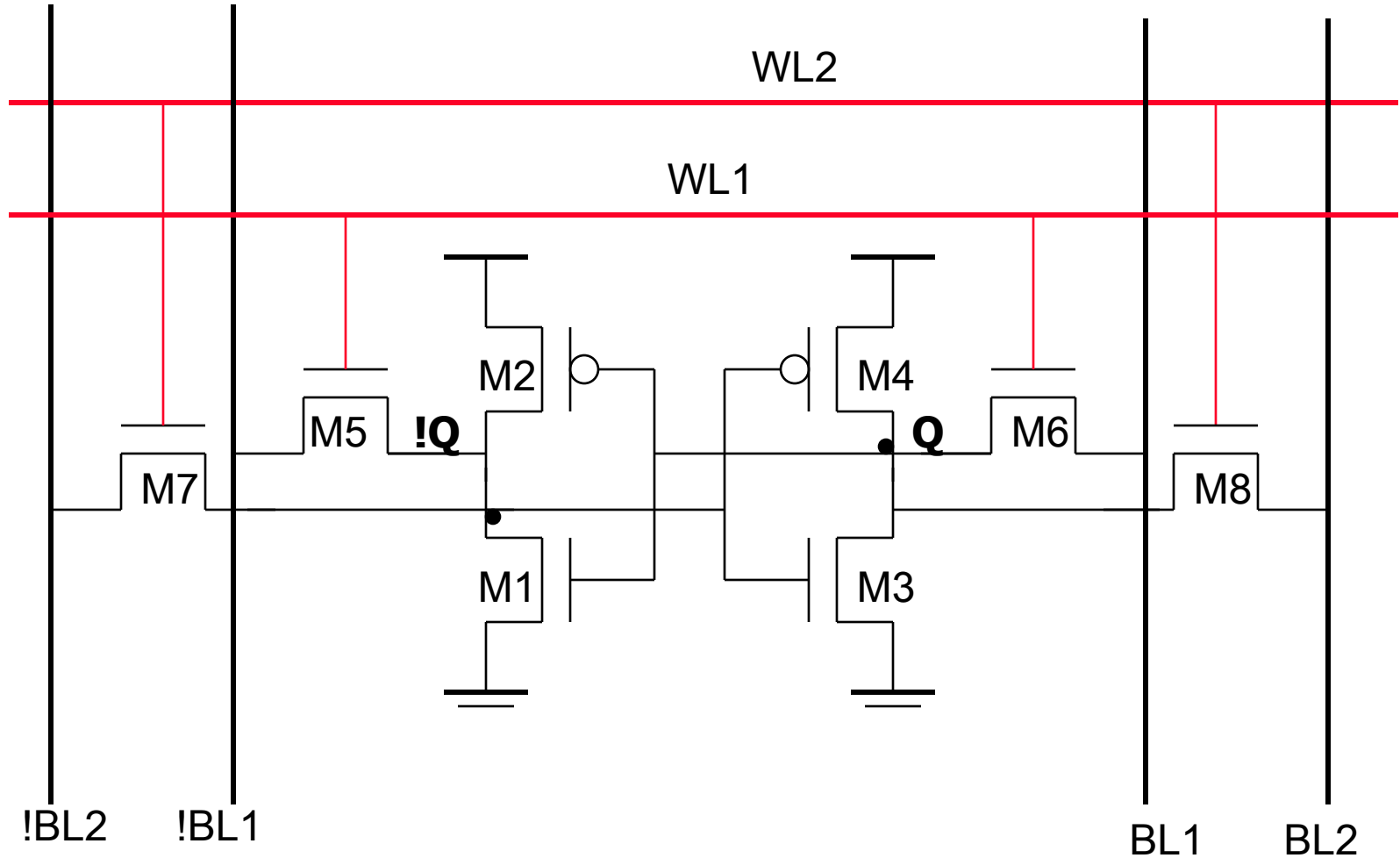

# 4x4 DRAM Memory

 

# 3-Transistor DRAM Cell

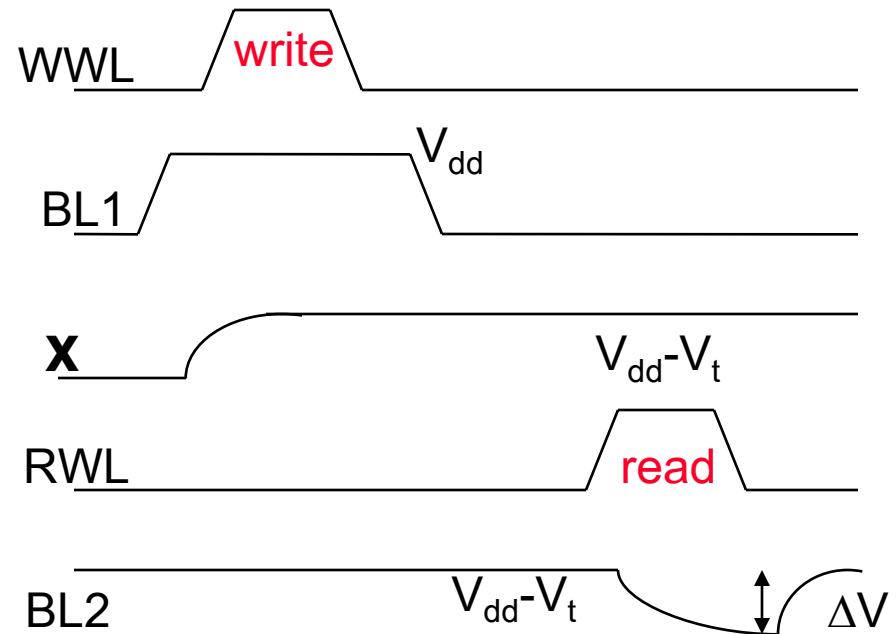 


No constraints on device sizes (ratioless)

Reads are non-destructive


Value stored at node X when writing a "1" is  $V_{WWL} - V_{tn}$

# 3T-DRAM Layout

 




# 1-Transistor DRAM Cell

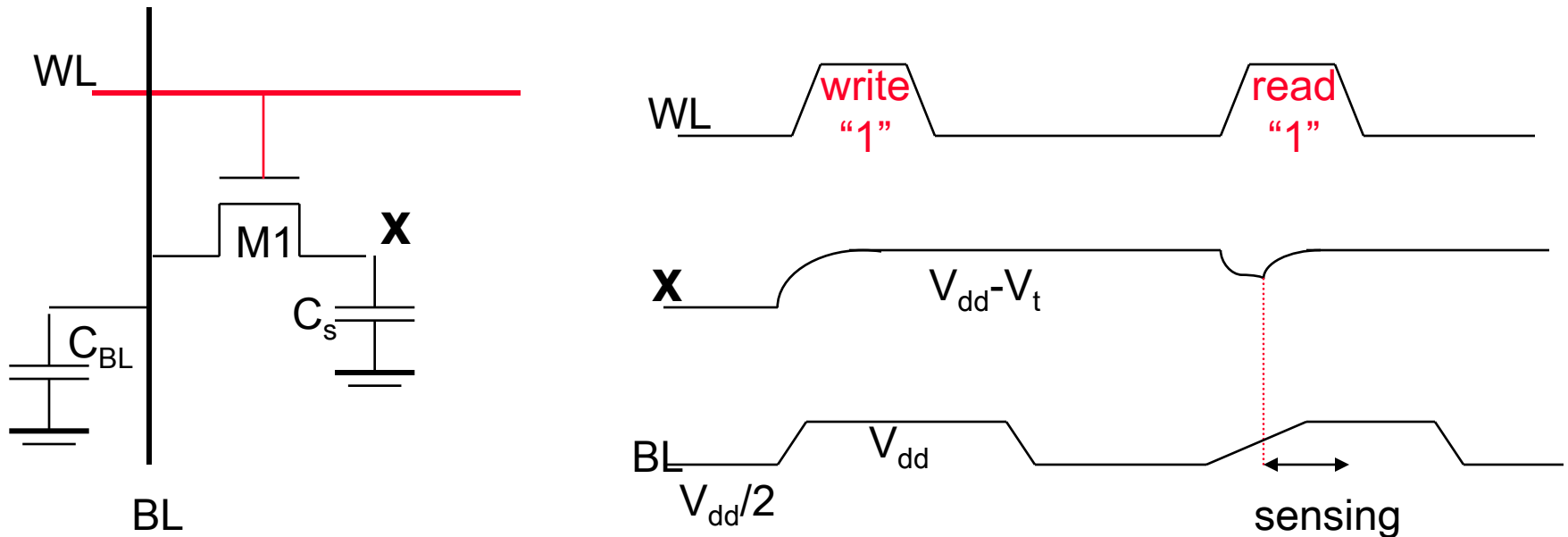


Write:  $C_s$  is charged (or discharged) by asserting WL and BL  
Read: Charge redistribution occurs between  $C_{BL}$  and  $C_s$

Read is destructive, so must refresh after read

# 1-T DRAM Cell

 

(a) Cross-section

 

(b) Layout

**Used Polysilicon-Diffusion Capacitance**  
**Expensive in Area**

# DRAM Cell Observations

---

- ❑ DRAM memory cells are single ended (complicates the design of the sense amp)
- ❑ 1T cell requires a sense amp for each bit line due to charge redistribution read
- ❑ 1T cell read is destructive; refresh must follow to restore data
- ❑ 1T cell requires an extra capacitor that must be explicitly included in the design
- ❑ A threshold voltage is lost when writing a 1 (can be circumvented by bootstrapping the word lines to a higher value than  $V_{dd}$ )

# Next Lecture and Reminders

---

## □ Next lecture

- Peripheral memory circuits
  - Reading assignment – Rabaey, et al, 12.3

## □ Reminders

- Project final reports due December 5<sup>th</sup>
- Final grading negotiations/correction (except for the final exam) must be concluded by December 10<sup>th</sup>
- Final exam scheduled
  - Monday, December 16<sup>th</sup> from 10:10 to noon in 118 and 121 Thomas