
CSE477

VLSI Digital Circuits


Fall 2002

Lecture 04: CMOS Inverter (static view)


Mary Jane Irwin (www.cse.psu.edu/~mji)
www.cse.psu.edu/~cg477

[Adapted from Rabaey's *Digital Integrated Circuits*, ©2002, J. Rabaey et al.]

Review: Design Abstraction Levels

 


Review: The MOS Transistor

 



CMOS Inverter:

A First Look

 

CMOS Inverter:

Steady State Response

  


$$\begin{aligned} V_{OL} &= 0 \\ V_{OH} &= V_{DD} \\ V_M &= f(R_n, R_p) \end{aligned}$$

CMOS Properties

- ❑ Full rail-to-rail swing \Rightarrow high noise margins
 - ❑ Logic levels not dependent upon the relative device sizes \Rightarrow transistors can be minimum size \Rightarrow ratioless
- ❑ Always a path to V_{dd} or GND in steady state \Rightarrow low output impedance (output resistance in $k\Omega$ range) \Rightarrow large fan-out (albeit with degraded performance)
- ❑ Extremely high input resistance (gate of MOS transistor is near perfect insulator) \Rightarrow nearly zero steady-state input current
- ❑ No direct path steady-state between power and ground \Rightarrow no static power dissipation
- ❑ Propagation delay function of load capacitance and resistance of transistors


Review: Short Channel I-V Plot (NMOS)

 

NMOS transistor, $0.25\mu\text{m}$, $L_d = 0.25\mu\text{m}$, $W/L = 1.5$, $V_{DD} = 2.5V$, $V_T = 0.4V$

Review: Short Channel I-V Plot (PMOS)

 - All polarities of all voltages and currents are reversed



PMOS transistor, $0.25\mu\text{m}$, $L_d = 0.25\mu\text{m}$, $W/L = 1.5$, $V_{DD} = 2.5V$, $V_T = -0.4V$



Transforming PMOS I-V Lines

- Want common coordinate set V_{in} , V_{out} , and I_{Dn}


$$I_{DSp} = -I_{DSn}$$

$$V_{GSn} = V_{in} ; V_{GSp} = V_{in} - V_{DD}$$
  
$$V_{DSn} = V_{out} ; V_{DSp} = V_{out} - V_{DD}$$




CMOS Inverter Load Lines

 



0.25um, $W/L_n = 1.5$, $W/L_p = 4.5$, $V_{DD} = 2.5V$, $V_{Tn} = 0.4V$, $V_{Tp} = -0.4V$

CMOS Inverter VTC

 

CMOS Inverter:

Switch Model of Dynamic Behavior

  

□ Gate response time is determined by the time to charge C_L through R_p (discharge C_L through R_n)

Relative Transistor Sizing

- ❑ When designing static CMOS circuits, balance the driving strengths of the transistors by making the PMOS section wider than the NMOS section to
 - ❑ maximize the noise margins and
 - ❑ obtain symmetrical characteristics

Switching Threshold

- V_M where $V_{in} = V_{out}$ (both PMOS and NMOS in saturation since $V_{DS} = V_{GS}$)

$$V_M \approx rV_{DD}/(1 + r) \text{ where } r = k_p V_{DSATp}/k_n V_{DSATn}$$

- Switching threshold set by the ratio r , which compares the **relative driving strengths** of the PMOS and NMOS transistors

- **Want** $V_M = V_{DD}/2$ (to have comparable high and low noise margins), so want $r \approx 1$

$$\frac{(W/L)_p}{(W/L)_n} = \frac{k_n' V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{k_p' V_{DSATp} (V_{DD} - V_M + V_{Tp} + V_{DSATp}/2)}$$

Switch Threshold Example


- ❑ In our generic 0.25 micron CMOS process, using the process parameters from slide L03.25, a $V_{DD} = 2.5V$, and a minimum size NMOS device ($(W/L)_n$ of 1.5)

	$V_{T0}(V)$	$\gamma(V^{0.5})$	$V_{DSAT}(V)$	$k'(A/V^2)$	$\lambda(V^{-1})$
NMOS	0.43	0.4	0.63	115×10^{-6}	0.06
PMOS	-0.4	-0.4	-1	-30×10^{-6}	-0.1

$$\frac{(W/L)_p}{(W/L)_n} = \frac{115 \times 10^{-6}}{-30 \times 10^{-6}} \times \frac{0.63}{-1.0} \times \frac{(1.25 - 0.43 - 0.63/2)}{(1.25 - 0.4 - 1.0/2)} = 3.5$$

$$(W/L)_p = 3.5 \times 1.5 = 5.25 \text{ for a } V_M \text{ of } 1.25V$$

Simulated Inverter V_M

 

Note: x-axis is semilog


□ V_M is relatively insensitive to variations in device ratio

● setting the ratio to 3, 2.5 and 2 gives V_M 's of 1.22V, 1.18V, and 1.13V


□ Increasing the width of the PMOS moves V_M towards V_{DD}

□ Increasing the width of the NMOS moves V_M toward GND

 Noise Margins Determining V_{IH} and V_{IL}



CMOS Inverter VTC from Simulation

 

$0.25\mu\text{m}$, $(W/L)_p/(W/L)_n = 3.4$
 $(W/L)_n = 1.5$ (min size)

$V_{DD} = 2.5\text{V}$

$V_M \approx 1.25\text{V}$, $g = -27.5$

$V_{IL} = 1.2\text{V}$, $V_{IH} = 1.3\text{V}$

$NM_L = NM_H = 1.2$

(actual values are

$V_{IL} = 1.03\text{V}$, $V_{IH} = 1.45\text{V}$


$NM_L = 1.03\text{V}$ & $NM_H = 1.05\text{V}$)

Output resistance

low-output = $2.4\text{k}\Omega$

high-output = $3.3\text{k}\Omega$

Gain Determinates

 


Gain is a strong function of the slopes of the currents in the saturation region, for $V_{in} = V_M$

$$g \approx \frac{(1+r)}{(V_M - V_{Tn} - V_{DSATn}/2)(\lambda_n - \lambda_p)}$$


Determined by technology parameters, especially channel length modulation (λ). Only designer influence through **supply voltage** and V_M (**transistor sizing**).

Impact of Process Variation on VTC Curve

 


□ Process variations (mostly) cause a shift in the switching threshold

Scaling the Supply Voltage

 


 Device threshold voltages are kept (virtually) constant



Device threshold voltages are kept (virtually) constant

Next Time: CMOS Inverter *max* Layout

 

Next Lecture and Reminders

❑ Next lecture

❑ IC manufacturing

- Reading assignment – Rabaey, et al, 2.1-2.3

❑ Reminders

❑ HW1 due September 10th (next lecture!)

❑ Project Title due September 12th (one week)

❑ Evening midterm exam scheduled

- Wednesday, October 10th from 8:15 to 10:15pm in 260 Willard
- Only one midterm conflict filed for so far