
CSE477

VLSI Digital Circuits

Fall 2002

Lecture 18: Dynamic Sequential Circuits

Mary Jane Irwin (www.cse.psu.edu/~mji)
www.cse.psu.edu/~cg477

[Adapted from Rabaey's *Digital Integrated Circuits*, ©2002, J. Rabaey et al.]

Review: Sequential Definitions


❑ Static versus dynamic storage

- ❑ static uses a **bistable** element with feedback (**regeneration**) and thus preserves its state as long as the power is on
- ❑ static is preferred when updates are infrequent (clock gating)
- ❑ dynamic stores state on parasitic capacitors so only holds the state for a period of time (milliseconds) and requires periodic refresh
- ❑ dynamic is usually simpler (fewer transistors), higher speed, lower power


❑ Latch versus flipflop

- ❑ latches are **level sensitive** with two modes: transparent - inputs are passed to Q and hold - output stable
- ❑ flipflops are **edge sensitive** that only sample the inputs on a clock transition

Review: Timing Metrics

 

Review: System Timing Constraints

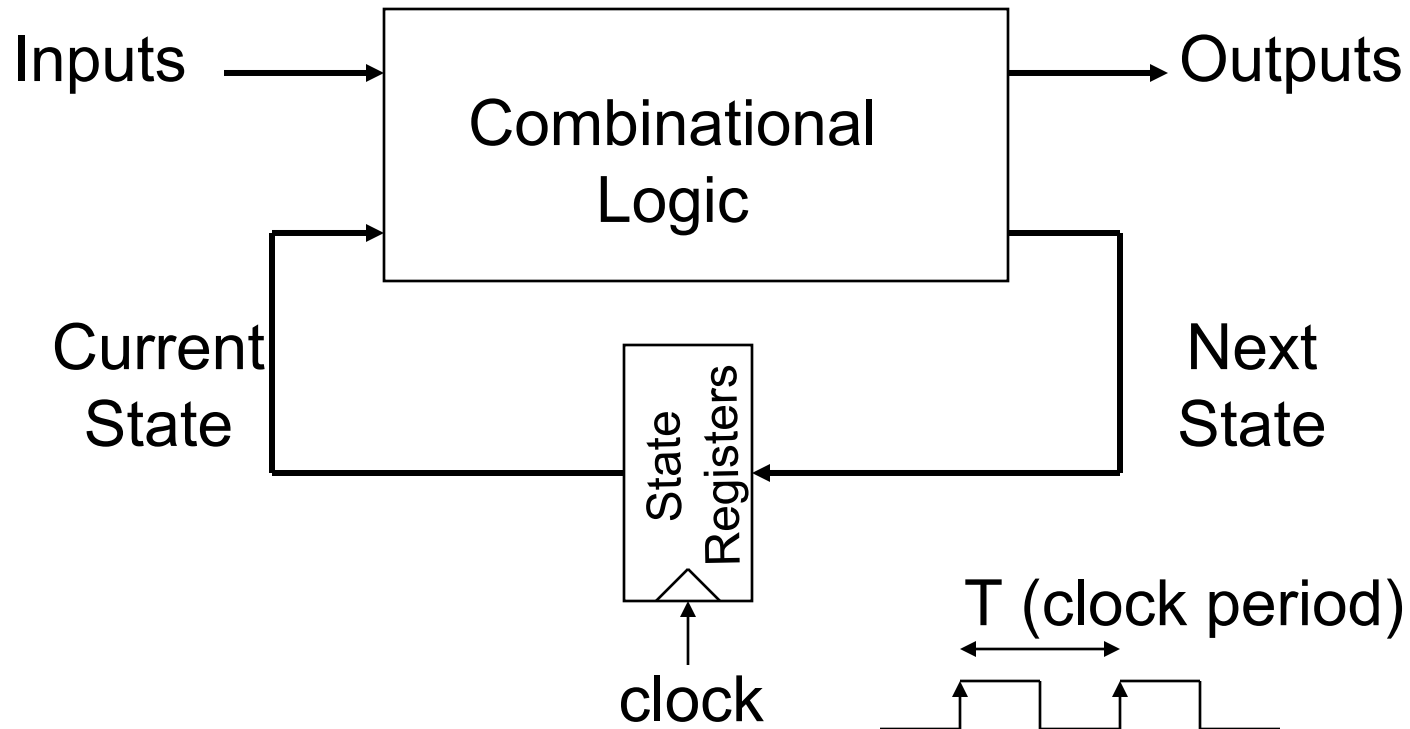


$$t_{\text{cdreg}} + t_{\text{cdlogic}} \geq t_{\text{hold}}$$

$$T \geq t_{\text{c-q}} + t_{\text{plogic}} + t_{\text{su}}$$


You spend all this time designing one machine and it's only a hot box for two years, and it has all the useful life of a washing machine.

The Soul of a New Machine, Kidder, pg. 239

Dynamic ET Flipflop

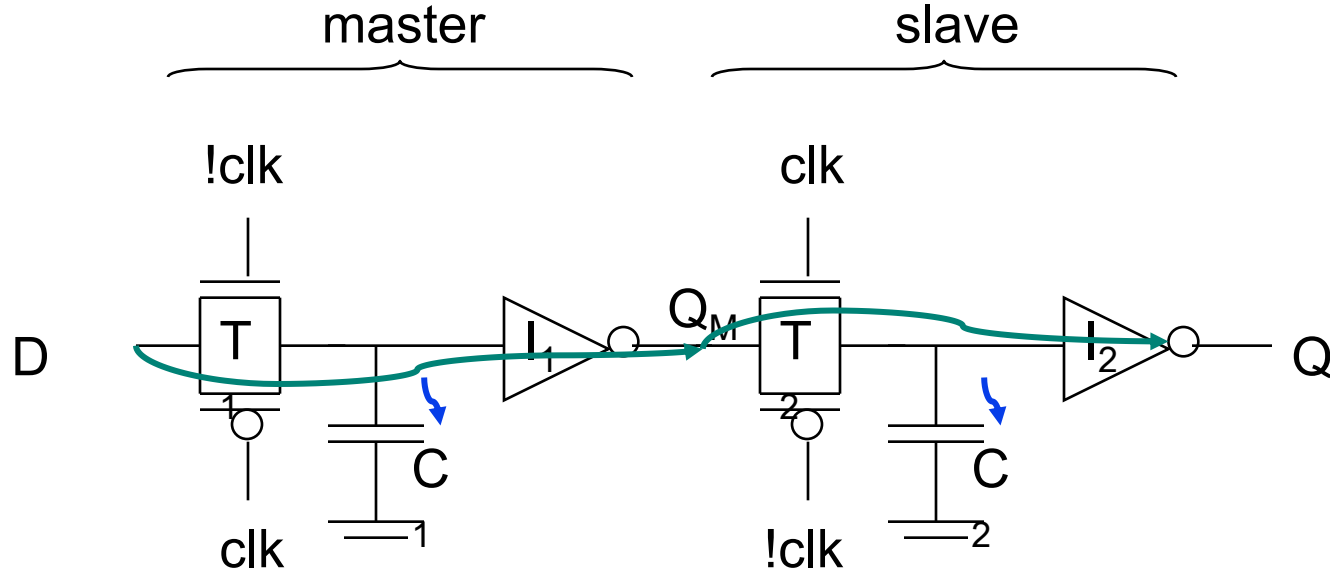



master transparent
slave hold

 

master hold
slave transparent

$$\begin{aligned}
 t_{su} &= t_{pd_tx} \\
 t_{hold} &= \text{zero} \\
 t_{c-q} &= 2 t_{pd_inv} + t_{pd_tx}
 \end{aligned}$$

Dynamic ET FF Race Conditions

  


0-0 overlap race condition

$$t_{\text{overlap0-0}} < t_{T1} + t_{I1} + t_{T2}$$


1-1 overlap race condition

$$t_{\text{overlap1-1}} < t_{\text{hold}}$$

Dynamic Two-Phase ET FF

 


master transparent
slave hold

 

master hold
slave transparent

Pseudostatic Dynamic Latch

 
- ❑ Robustness considerations limit the use of dynamic FF's
 - ❑ coupling between signal nets and internal storage nodes can inject significant noise and destroy the FF state
 - ❑ leakage currents cause state to leak away with time
 - ❑ internal dynamic nodes don't track fluctuations in V_{DD} that reduces noise margins
- ❑ A simple fix is to make the circuit **pseudostatic**




- ❑ Add above logic added to all dynamic latches

C²MOS (Clocked CMOS) ET Flipflop

- ❑ A clock-skew insensitive FF

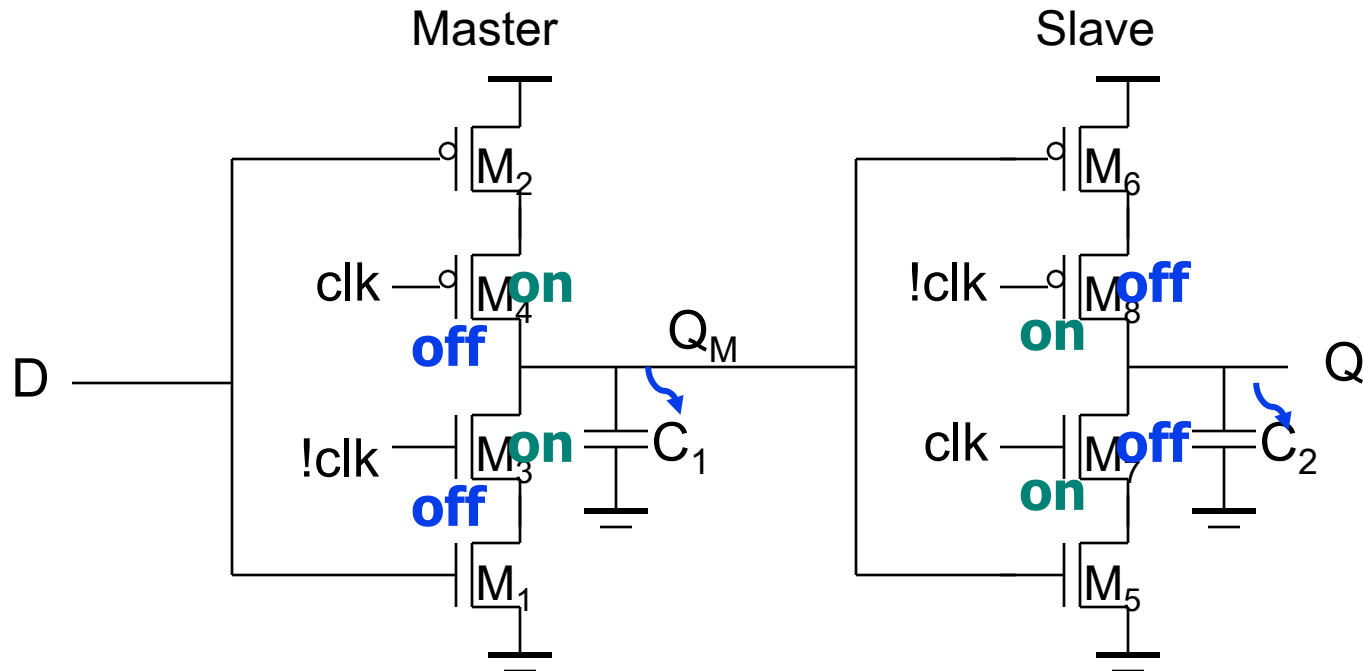


master transparent
slave hold

 


C²MOS FF 0-0 Overlap Case

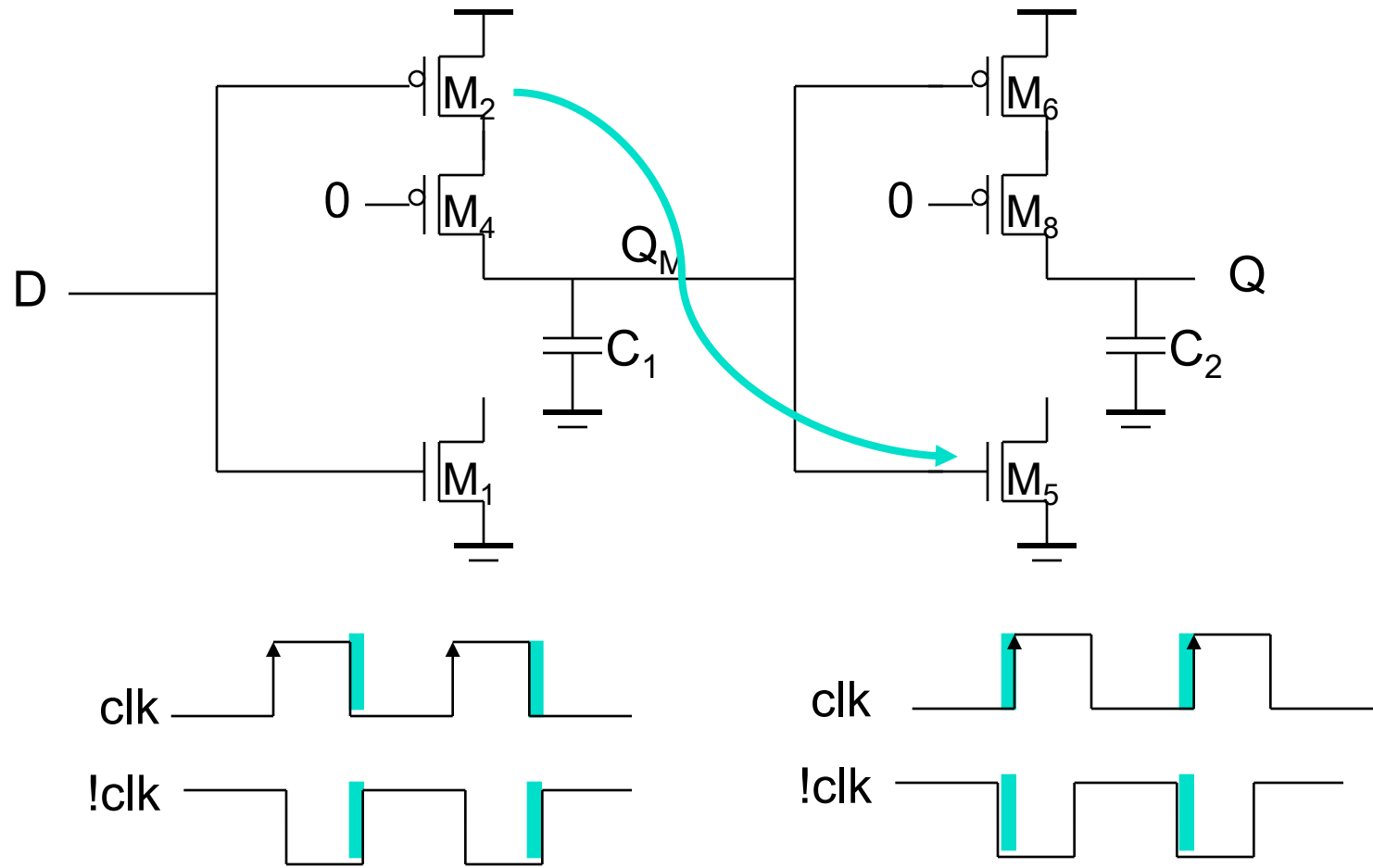- ❑ Clock-skew insensitive as long as the rise and fall times of the clock edges are sufficiently small




C²MOS FF 1-1 Overlap Case

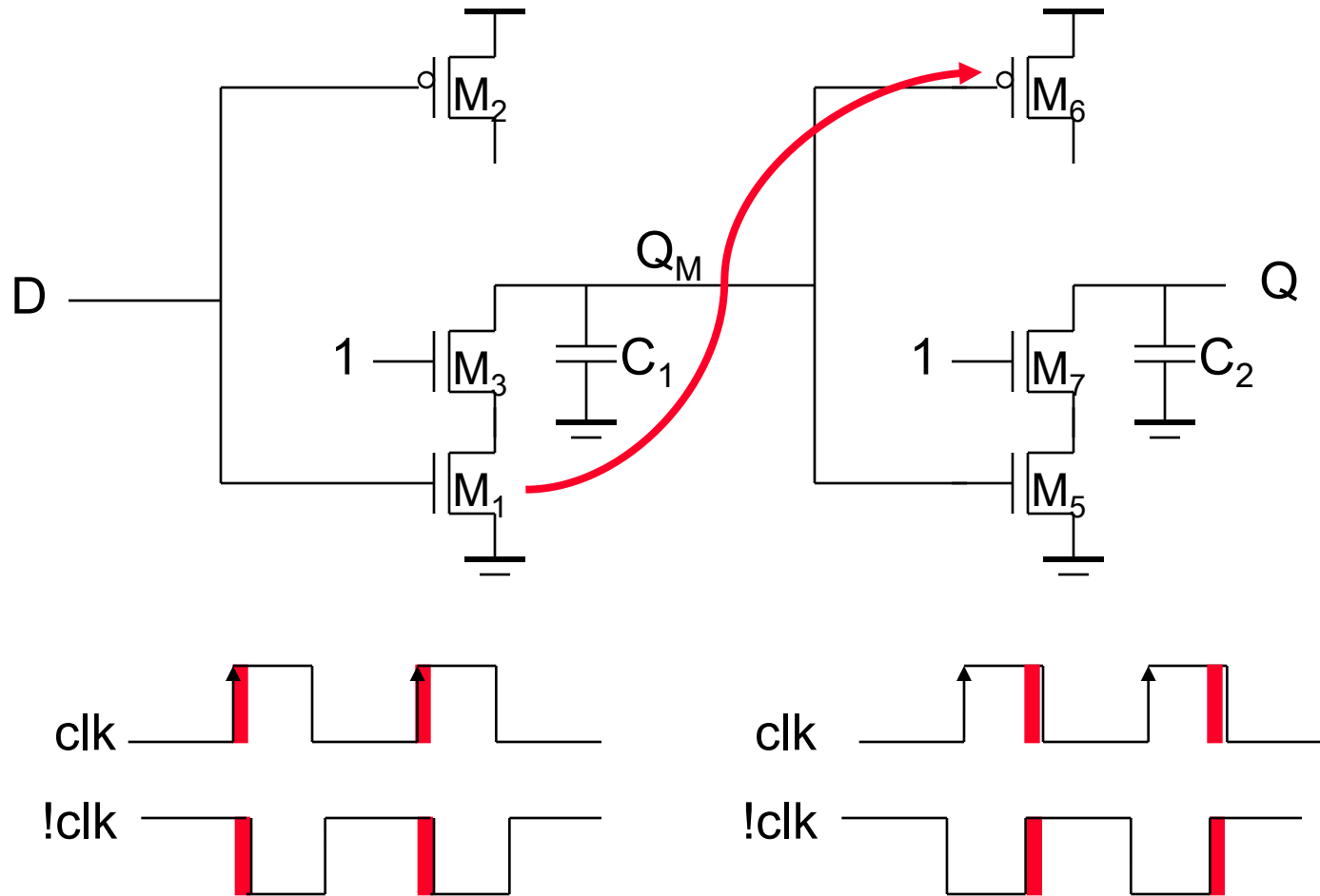

1-1 overlap constraint

$$t_{\text{overlap1-1}} < t_{\text{hold}}$$

C²MOS Transient Response

 


For a
0.1 ns clock

For a
3 ns clock
(race condition
exists)


True Single Phase Clocked (TSPC) Latches

Negative Latch

 


hold when $\text{clk} = 1$
transparent when $\text{clk} = 0$

Positive Latch

 


transparent when $\text{clk} = 1$
hold when $\text{clk} = 0$


TSPC ET FF

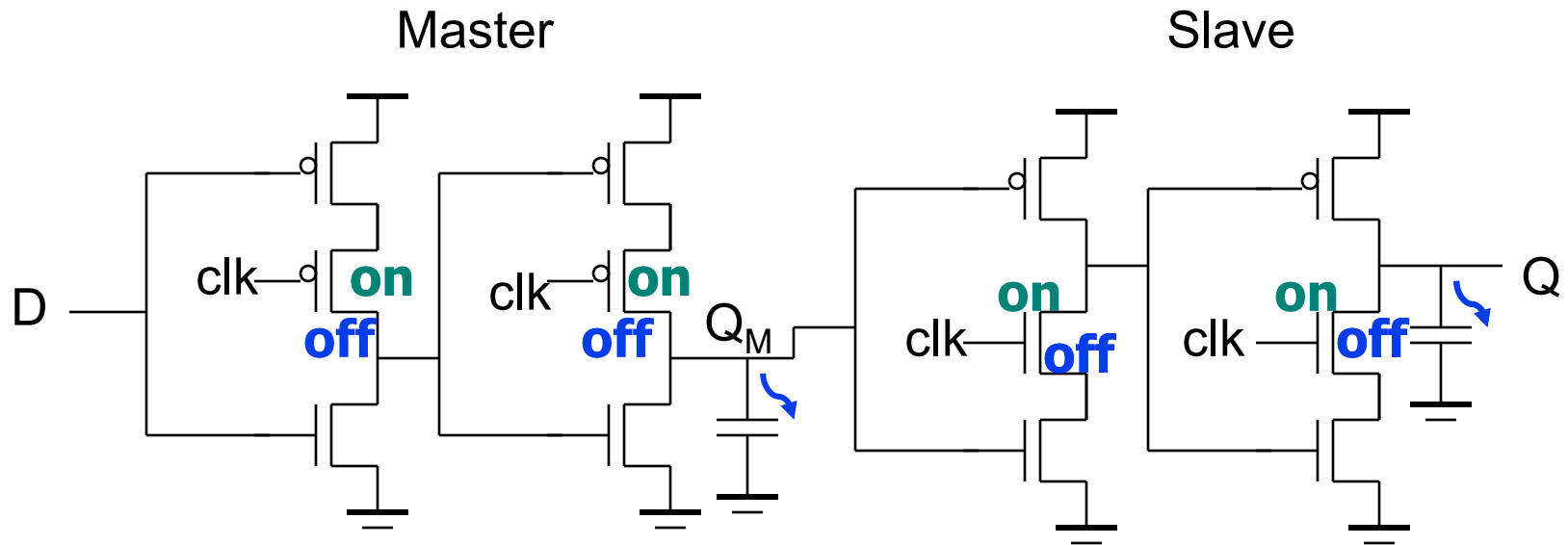


master transparent
slave hold

 


Simplified TSPC ET FF

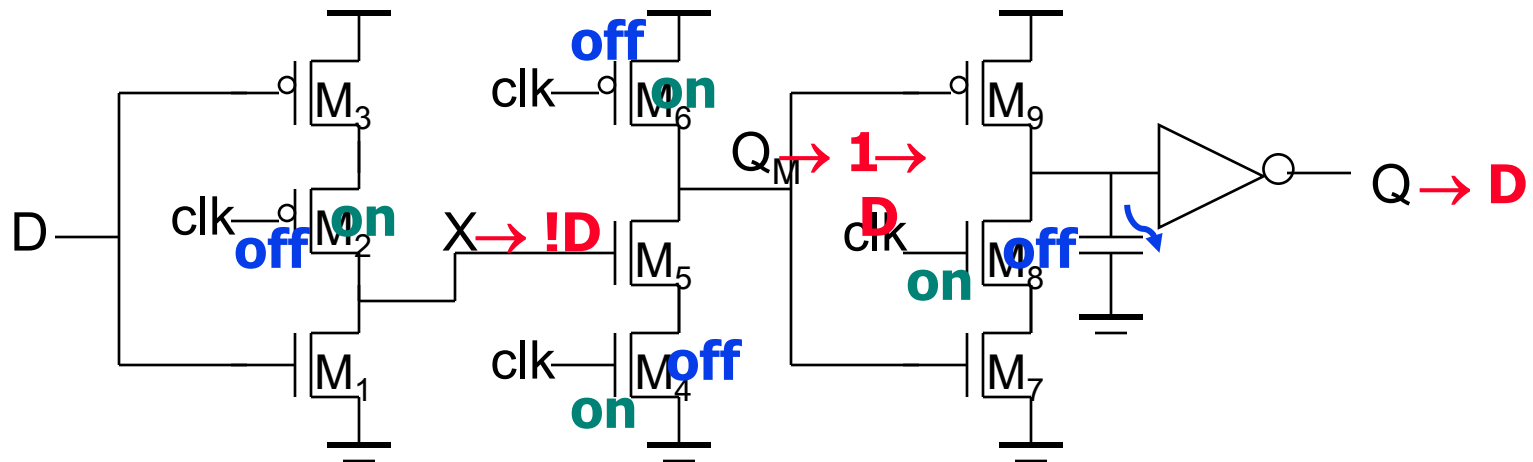

master transparent
slave hold

 

Sizing Issues in Simplified TSPC ET FF

 

Transistor sizing

Original width

$M_4, M_5 = 0.5\mu\text{m}$

$M_7, M_8 = 2\mu\text{m}$


Modified width

$M_4, M_5 = 1\mu\text{m}$

$M_7, M_8 = 1\mu\text{m}$

Split-Output TSPC Latches

Positive Latch

 


transparent when $\text{clk} = 1$

hold when $\text{clk} = 0$

When $\text{In} = 0$, $A = V_{DD} - V_{Tn}$

Negative Latch


 


hold when $\text{clk} = 1$

transparent when $\text{clk} = 0$


When $\text{In} = 1$, $A = |V_{Tp}|$

Split-Output TSPC ET FF

  


Pulsed FF (AMD-K6)

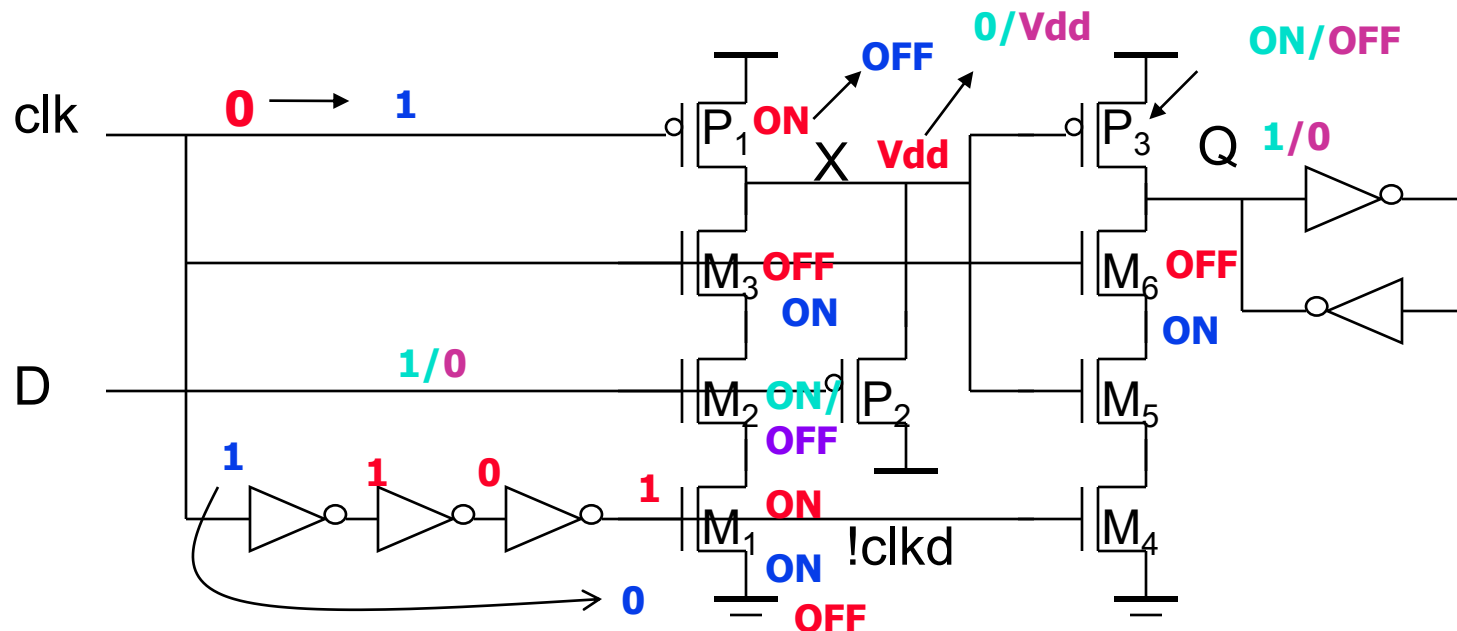- ❑ Pulse registers - a short pulse (**glitch clock**) is generated locally from the rising (or falling) edge of the system clock and is used as the clock input to the flipflop
 - ❑ race conditions are avoided by keeping the transparent mode time very short (during the pulse only)
 - ❑ advantage is reduced clock load; disadvantage is substantial increase in verification complexity



Sense Amp FF (StrongArm SA100)

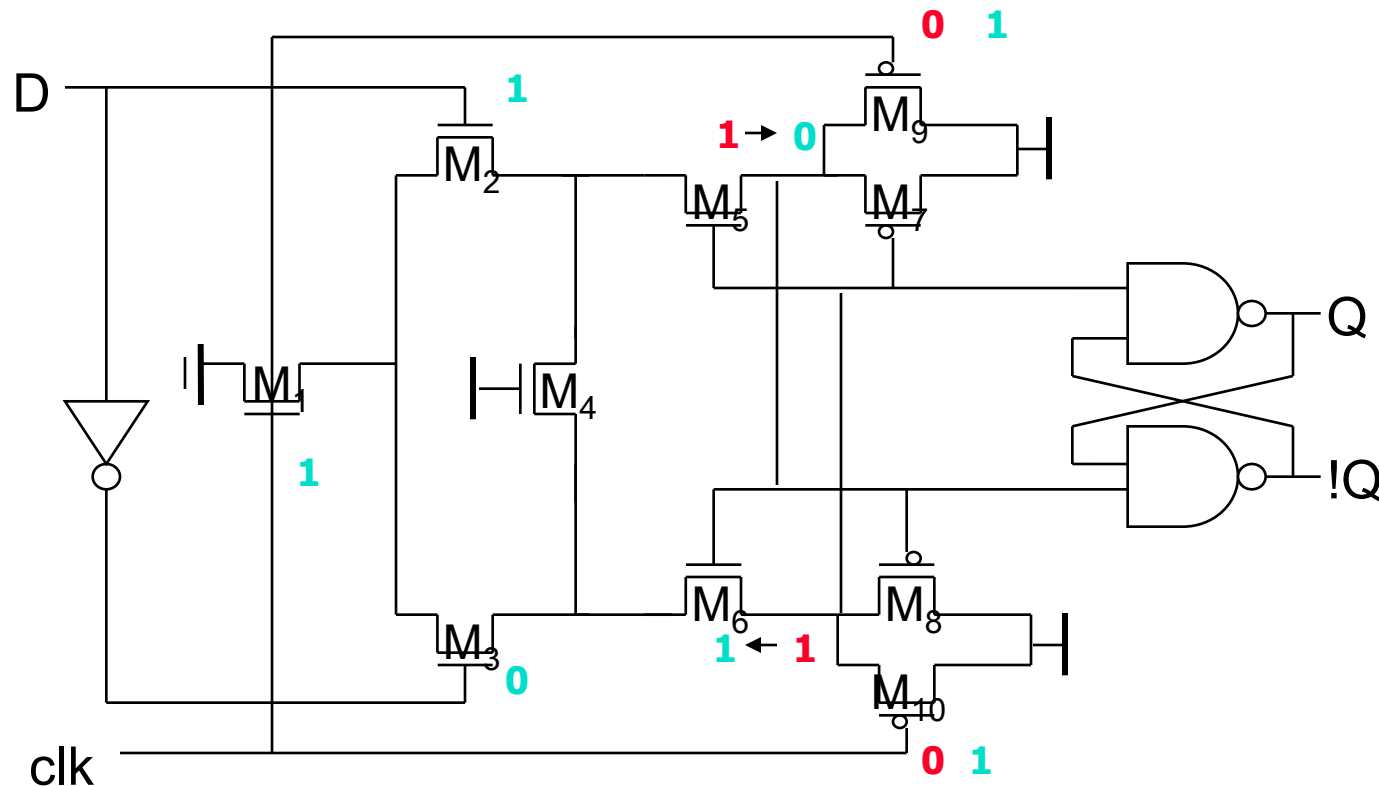- ❑ Sense amplifier (circuits that accept small swing input signals and amplify them to full rail-to-rail signals) flipflops
 - ❑ advantages are reduced clock load and that it can be used as a receiver for reduced swing differential buses



Flipflop Comparison Chart

Name	Type	#clk Id	#tr	$t_{\text{set-up}}$	t_{hold}	t_{pFF}
Mux	Static	8 (clk-!clk)	20	$3t_{\text{pinv}} + t_{\text{ptx}}$	0	$t_{\text{pinv}} + t_{\text{ptx}}$
PowerPC	Static	8 (clk-!clk)	16			
2-phase	Ps-Static	8 (clk1-clk2)	16			
T-gate	Dynamic	4 (clk-!clk)	8	t_{ptx}	$t_{\text{o1-1}}$	$2t_{\text{pinv}} + t_{\text{ptx}}$
C ² MOS	Dynamic	4 (clk-!clk)	8			
TSPC	Dynamic	4 (clk)	11	t_{pinv}	t_{pinv}	$3t_{\text{pinv}}$
S-O TSPC	Dynamic	2 (clk)	10			
AMD K6	Dynamic	5 (clk)	19			
SA 100	SenseAmp	3 (clk)	20			

Choosing a Clocking Strategy

- ❑ Choosing the right clocking scheme affects the functionality, speed, and power of a circuit
- ❑ Two-phase designs
 - ❑ + robust and conceptually simple
 - ❑ - need to generate and route two clock signals
 - ❑ - have to design to accommodate possible skew between the two clock signals
- ❑ Single phase designs
 - ❑ + only need to generate and route one clock signal
 - ❑ + supported by most automated design methodologies
 - ❑ + don't have to worry about skew between the two clocks
 - ❑ - have to have guaranteed slopes on the clock edges

Next Lecture and Reminders

□ Next lecture

- Timing issues, Intro to datapath design
 - Reading assignment – Rabaey, et al, 10.1-10.3.3; 11.1-11.2

□ Reminders

- Pick up second half of the new edition of the book from Sue in 202 Pond Lab
- Project final reports due December 5th
- HW4 due November 5th
- HW5 out November 5th and due November 19th
- Final exam scheduled
 - Monday, December 16th from 10:10 to noon in TBD