

---

# **CSE477**

## **VLSI Digital Circuits**

### **Fall 2002**

## **Lecture 21: Multiplier Design**

Mary Jane Irwin ( [www.cse.psu.edu/~mji](http://www.cse.psu.edu/~mji) )  
[www.cse.psu.edu/~cg477](http://www.cse.psu.edu/~cg477)

[Adapted from Rabaey's *Digital Integrated Circuits*, ©2002, J. Rabaey et al.]

# Review: Basic Building Blocks

---

## ❑ Datapath

- ❑ Execution units
  - Adder, multiplier, divider, shifter, etc.
- ❑ Register file and pipeline registers
- ❑ Multiplexers, decoders

## ❑ Control

- ❑ Finite state machines (PLA, ROM, random logic)


## ❑ Interconnect

- ❑ Switches, arbiters, buses

## ❑ Memory


- ❑ Caches (SRAMs), TLBs, DRAMs, buffers

# Review: Binary Adder Landscape

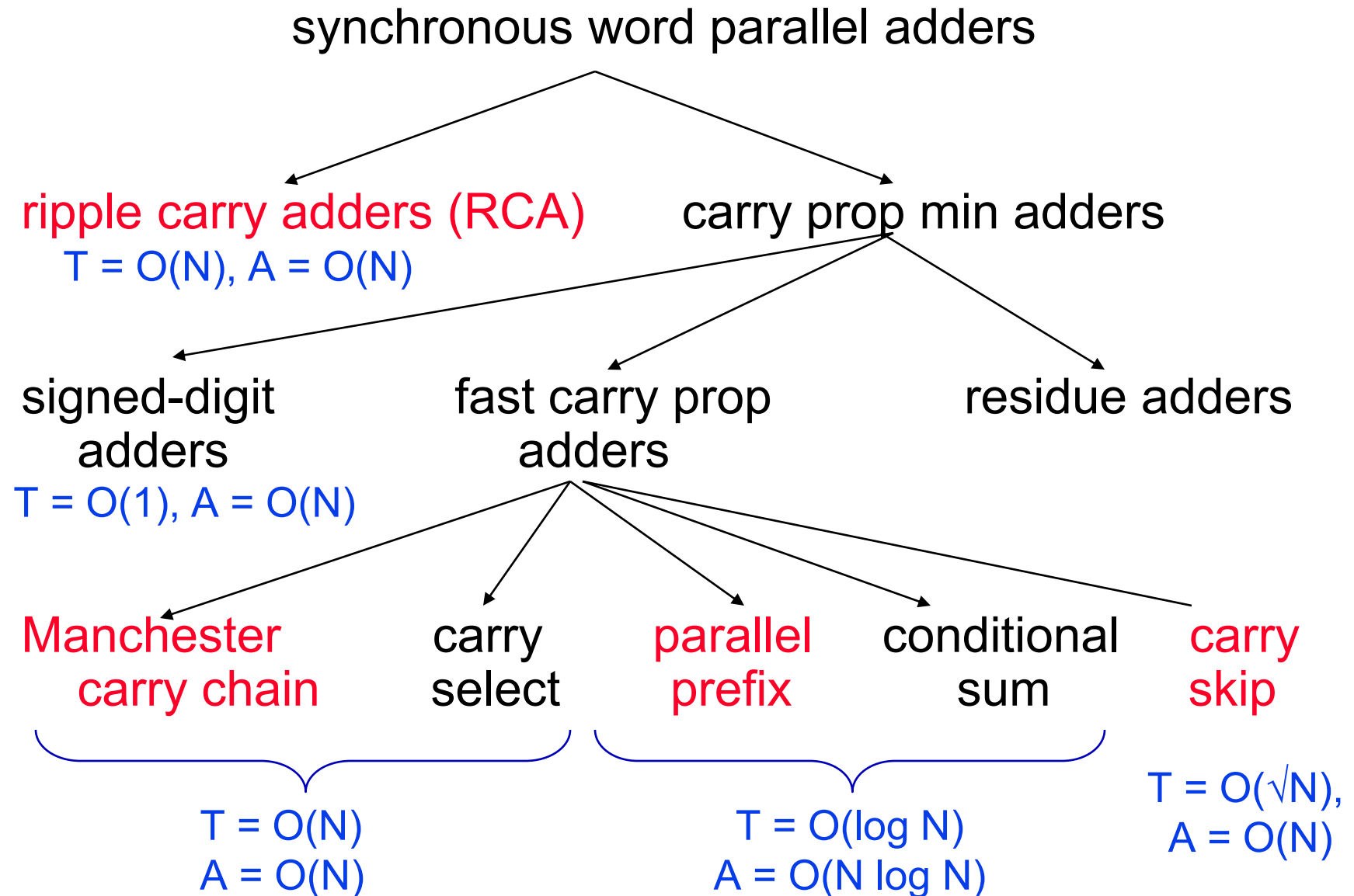

# Multiply Operation

- ❑ Multiplication as repeated additions

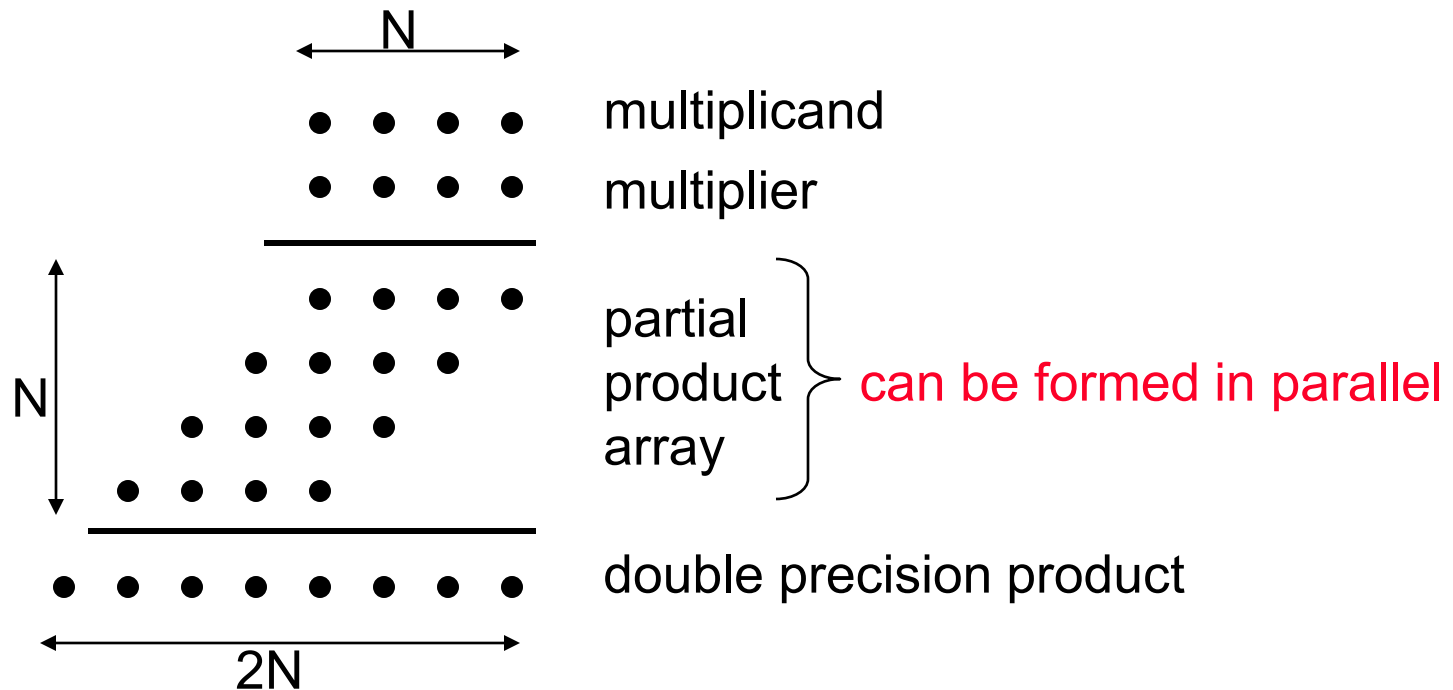

# Shift & Add Multiplication

---

## ❑ Right shift and add

- ❑ Partial product array rows are accumulated from top to bottom on an N-bit adder
- ❑ After each addition, right shift (by one bit) the accumulated partial product to align it with the next row to add
- ❑ Time for N bits  $T_{\text{serial\_mult}} = O(N T_{\text{adder}}) = O(N^2)$  for a RCA


## ❑ Making it faster

- ❑ Use a faster adder
- ❑ Use higher radix (e.g., base 4) multiplication
  - Use **multiplier recoding** to simplify multiple formation
- ❑ Form partial product array in parallel and add it in parallel


## ❑ Making it smaller (i.e., slower)

- ❑ Use an array multiplier
  - Very regular structure with only short wires to nearest neighbor cells. Thus, very simple and efficient layout in VLSI
  - Can be easily and efficiently pipelined


# Tree Multiplier Structure

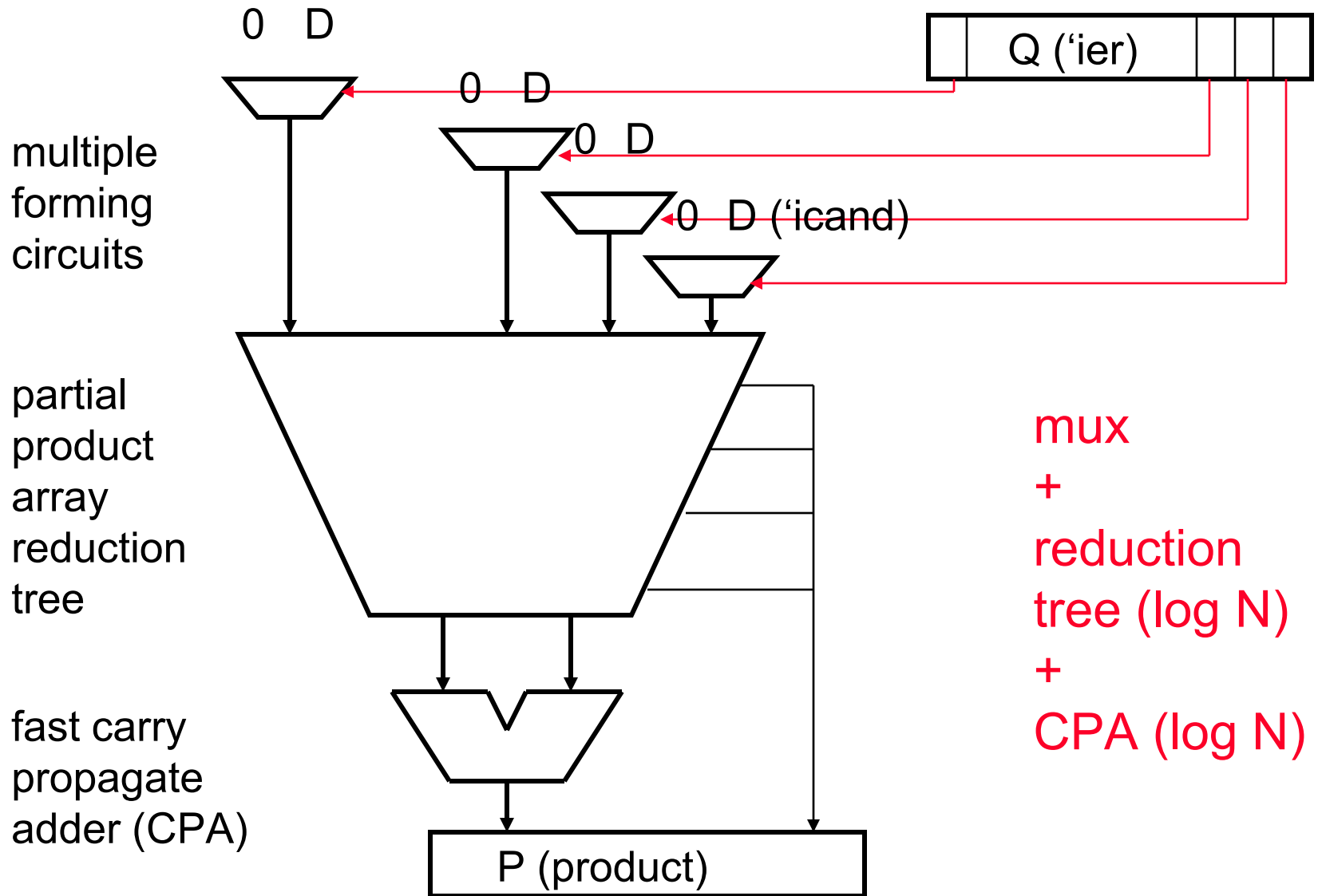

# (4,2) Counter

 


 - ❑ Built out of two (3,2) counters (just FA's!)
  - ❑ all of the inputs (4 external plus one internal) have the same weight (i.e., are in the **same** bit position)
  - ❑ the internal output is carried to the next higher weight position (indicated by the  $\leftarrow$  )



Note: **Two** carry outs - one “internal” and one “external”

# Tiling (4,2) Counters

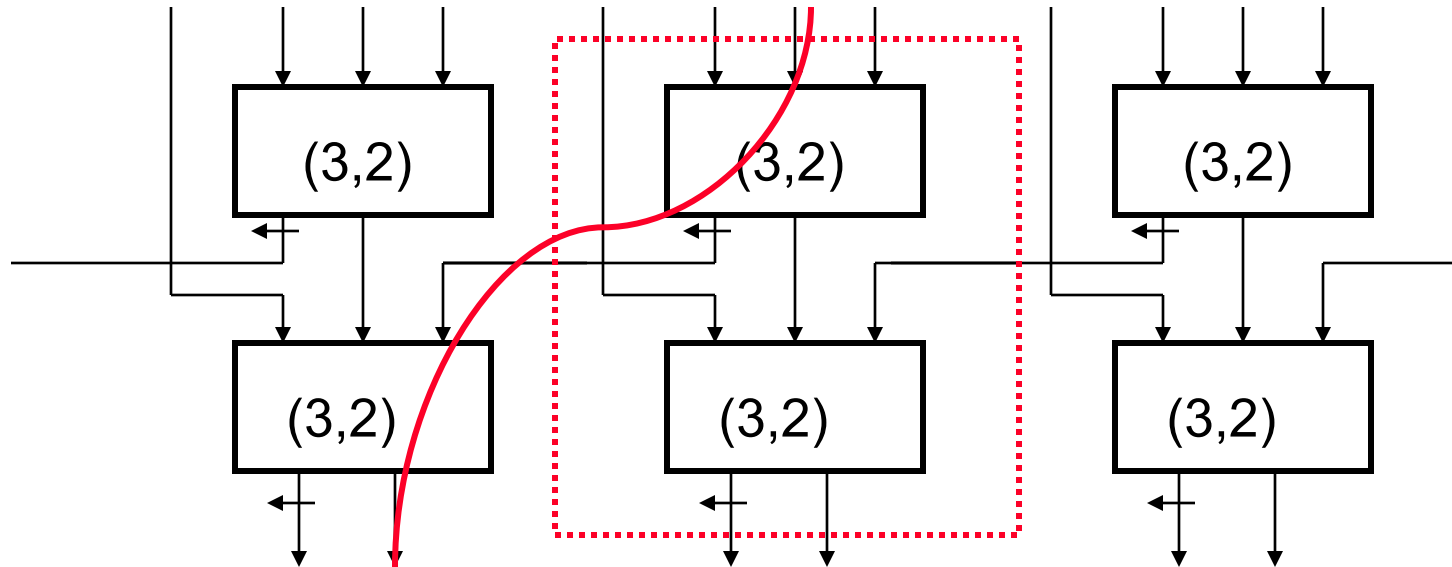


- ❑ Reduces columns **four** high to columns only **two** high
  - ❑ Tiles with neighboring (4,2) counters
  - ❑ Internal carry in at same “level” (i.e., bit position weight) as the internal carry out



 
# 4x4 Partial Product Array Reduction

- Fast 4x4 multiplication using (4,2) counters


 
# 8x8 Partial Product Array Reduction

How many  
(4,2)  
counters  
*minimum*  
are needed  
to reduce it  
to 2 rows?




**Answer: 24**


# Alternate 8x8 Partial Product Array
 
## Reduction

More (4,2)  
counters, so  
what is the  
advantage?



# Array Reduction Layout Approach

 

# Next Lecture and Reminders

---

## □ Next lecture

- Shifters, decoders, and multiplexers
  - Reading assignment – Rabaey, et al, 11.5-11.6

## □ Reminders

- Project final reports due December 5<sup>th</sup>
- HW5 (last one!) due November 19<sup>th</sup>
- Final grading negotiations/correction (except for the final exam) must be concluded by December 10<sup>th</sup>
- Final exam scheduled
  - Monday, December 16<sup>th</sup> from 10:10 to noon in 118 and 121 Thomas