
CSE477

VLSI Digital Circuits


Fall 2002

Lecture 06: Static CMOS Logic

Mary Jane Irwin (www.cse.psu.edu/~mji)
www.cse.psu.edu/~cg477

[Adapted from Rabaey's *Digital Integrated Circuits*, ©2002, J. Rabaey et al.]

Review: CMOS Process at a Glance

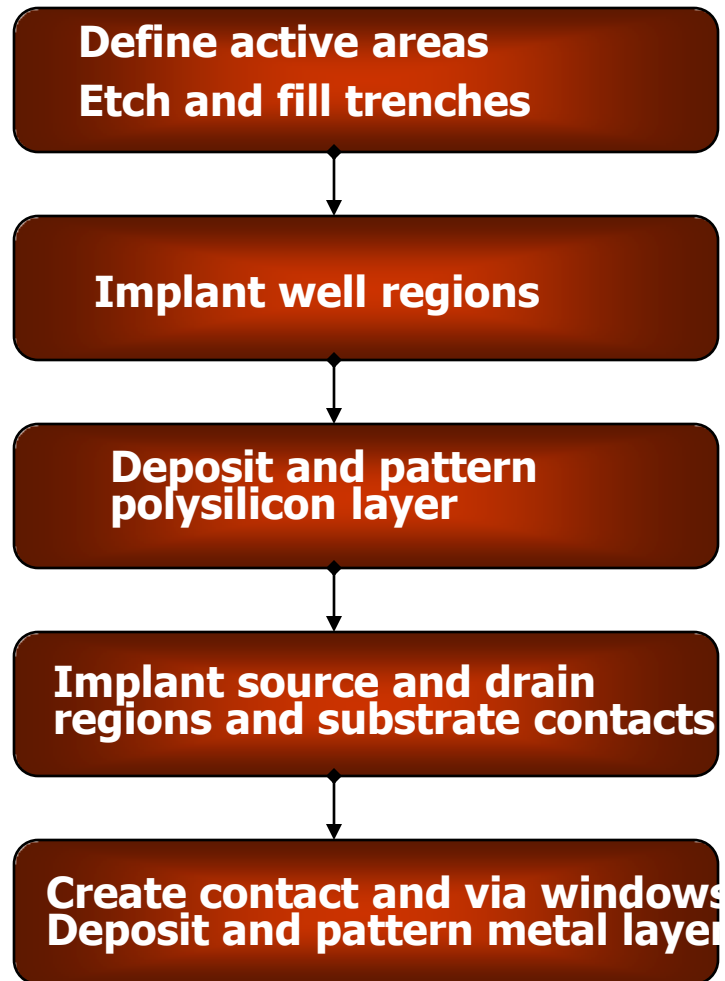


- ❑ One full **photolithography** sequence per layer (mask)
 - ❑ Built (roughly) from the bottom up
- 4 **metal**
- 2 **polysilicon**
- 3 **source and drain diffusions**
- 1 **tubs (aka wells, active areas)**
- exception!

CMOS Circuit Styles

- ❑ **Static complementary** CMOS - except during switching, output connected to either V_{DD} or GND via a low-resistance path
 - ❑ high noise margins
 - full rail to rail swing
 - V_{OH} and V_{OL} are at V_{DD} and GND, respectively
 - ❑ low output impedance, high input impedance
 - ❑ no steady state path between V_{DD} and GND (**no** static power consumption)
 - ❑ delay a function of load capacitance and transistor resistance
 - ❑ comparable rise and fall times (under the appropriate transistor sizing conditions)
- ❑ **Dynamic** CMOS - relies on temporary storage of signal values on the capacitance of high-impedance circuit nodes
 - ❑ simpler, faster gates
 - ❑ increased sensitivity to noise

Static Complementary CMOS


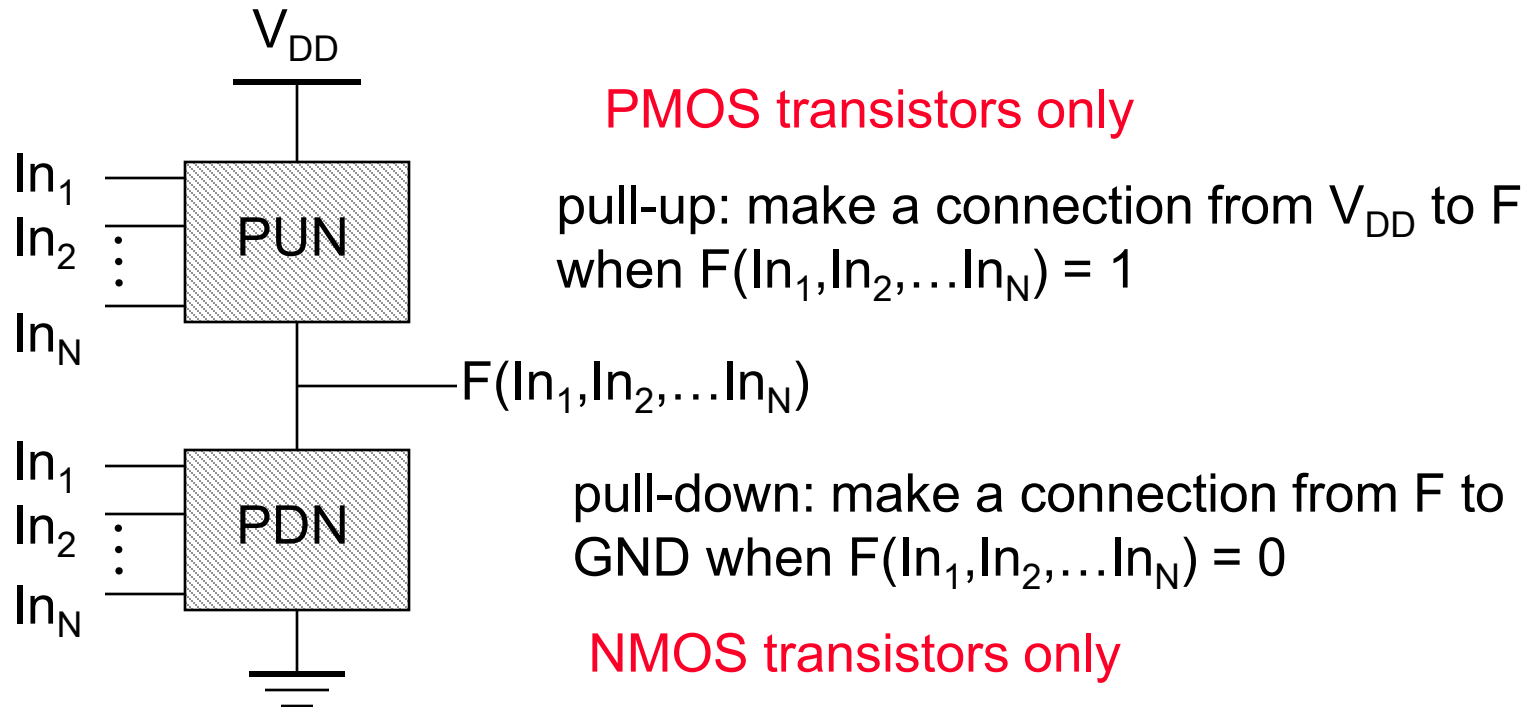
- ❑ Pull-up network (PUN) and pull-down network (PDN)





PUN and PDN are **dual** logic networks

Threshold Drops

PUN

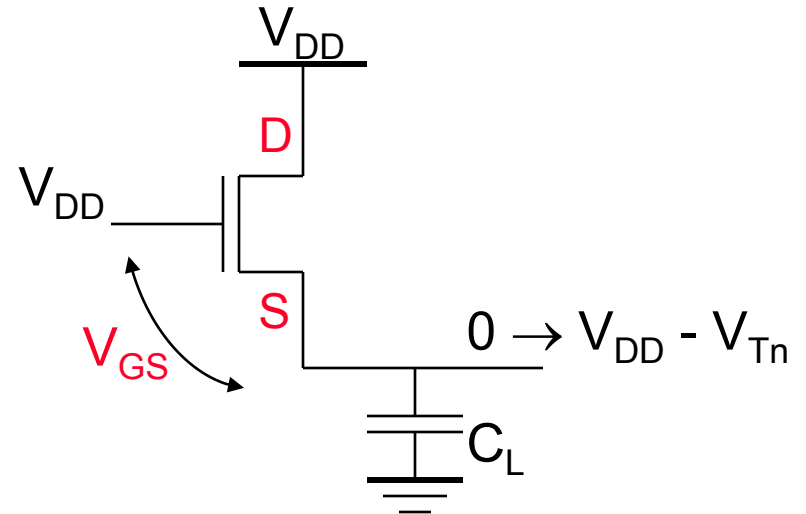 


PDN

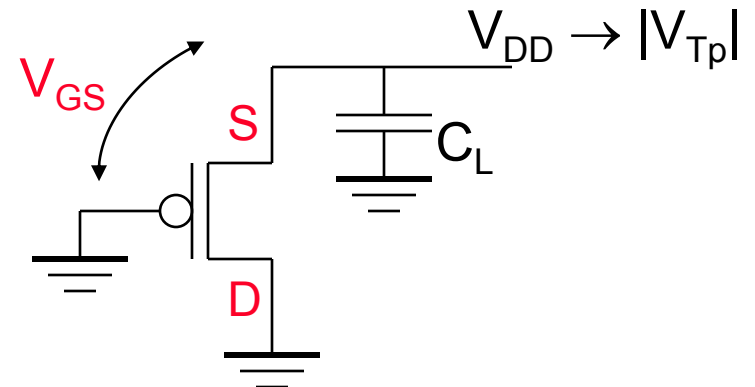 


Construction of PDN

 - NMOS devices in **series** implement a NAND function



 - NMOS devices in **parallel** implement a NOR function



Dual PUN and PDN

- PUN and PDN are dual networks


- DeMorgan's theorems

$$\overline{A + B} = \overline{A} \cdot \overline{B} \quad [!(A + B) = !A \cdot !B \text{ or } !(A | B) = !A \& !B]$$


$$\overline{A \cdot B} = \overline{A} + \overline{B} \quad [!(A \cdot B) = !A + !B \text{ or } !(A \& B) = !A | !B]$$

- a **parallel** connection of transistors in the PUN corresponds to a **series** connection of the PDN
- Complementary gate is naturally **inverting** (NAND, NOR, AOI, OAI)
- Number of transistors for an N-input logic gate is **2N**


CMOS NAND

 


A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

 


CMOS NOR

 


A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

 

Complex CMOS Gate


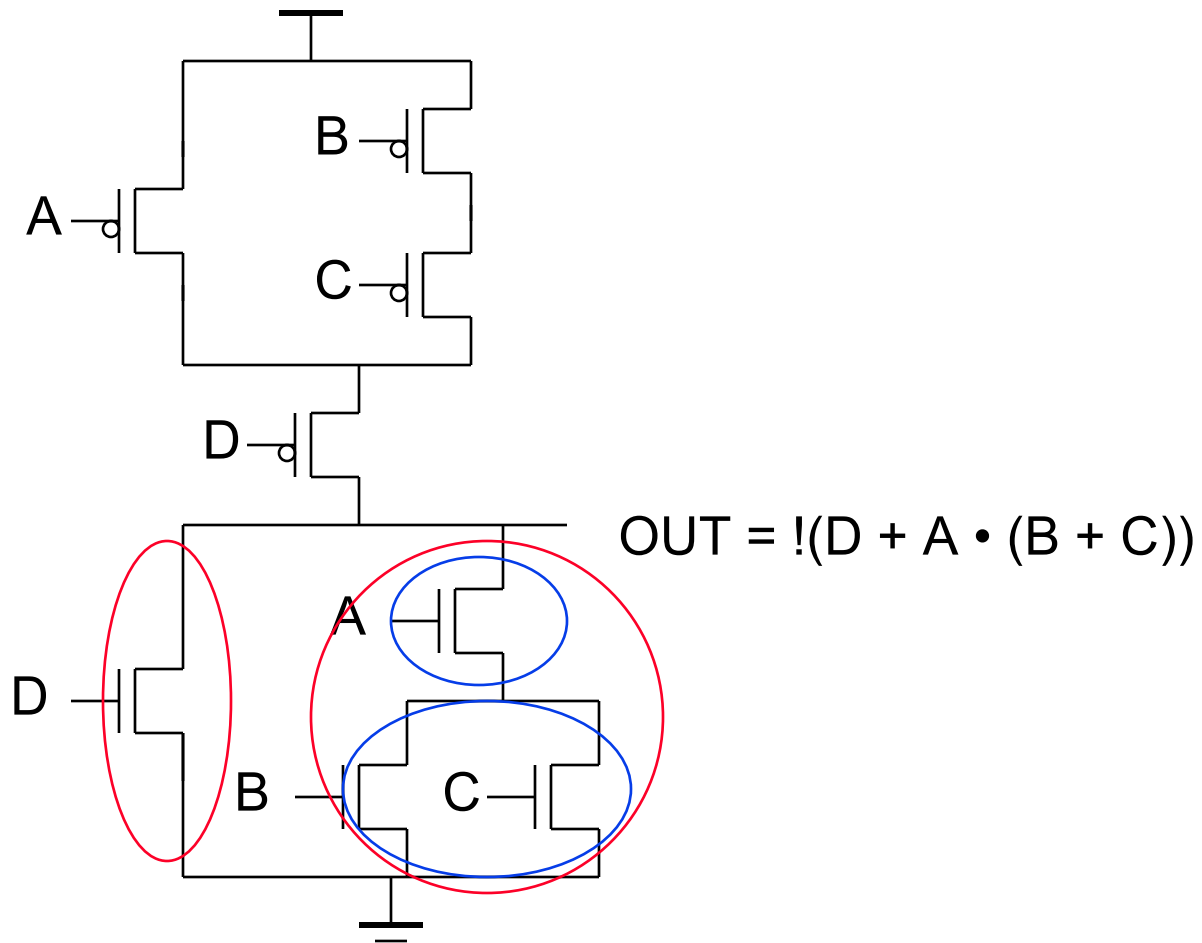


Standard Cell Layout Methodology

 


What logic function is this?

OAI21 Logic Graph

  


 Two Stick Layouts of $!(C \cdot (A + B))$





Consistent Euler Path

 - ❑ An uninterrupted diffusion strip is possible only if there exists a Euler path in the logic graph
 - ❑ Euler path: a path through all nodes in the graph such that each edge is visited once and only once.




- ❑ For a single poly strip for every input signal, the Euler paths in the PUN and PDN must be **consistent** (the same)

OAI22 Logic Graph

 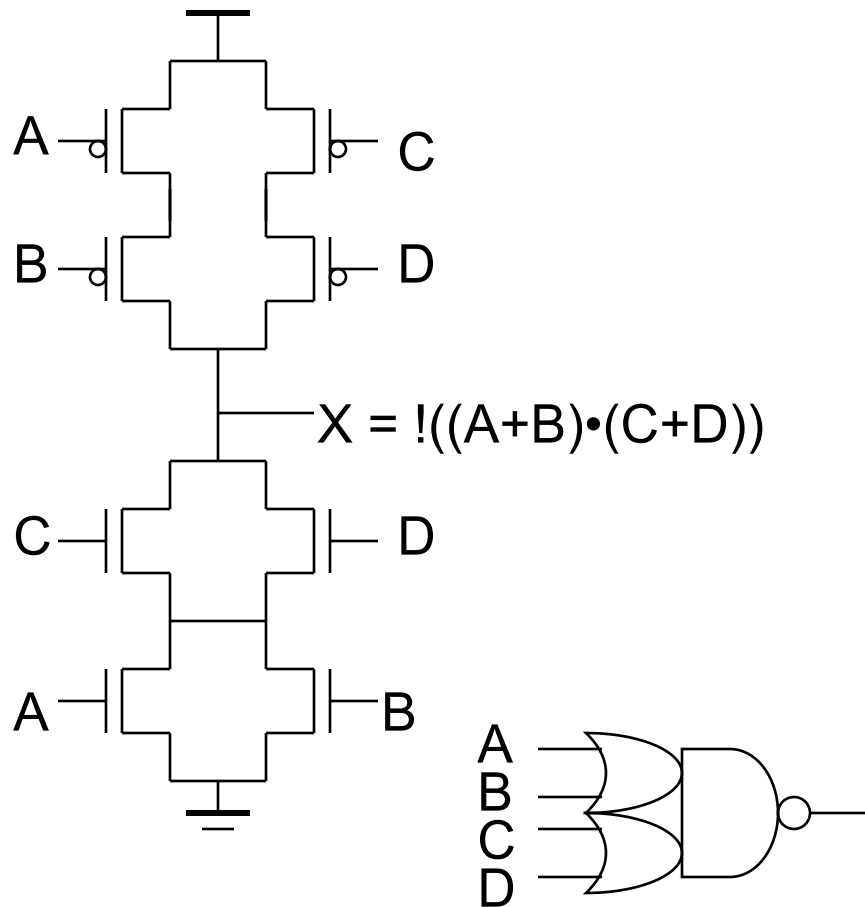


OAI22 Layout

 




- ❑ Some functions have no consistent Euler path like $x = !(a + bc + de)$ (but $x = !(bc + a + de)$ does!)

XNOR/XOR Implementation

XNOR


 


XOR

   

- ❑ How many transistors in each?
- ❑ Can you create the stick transistor layout for the lower left circuit?

VTC is Data-Dependent

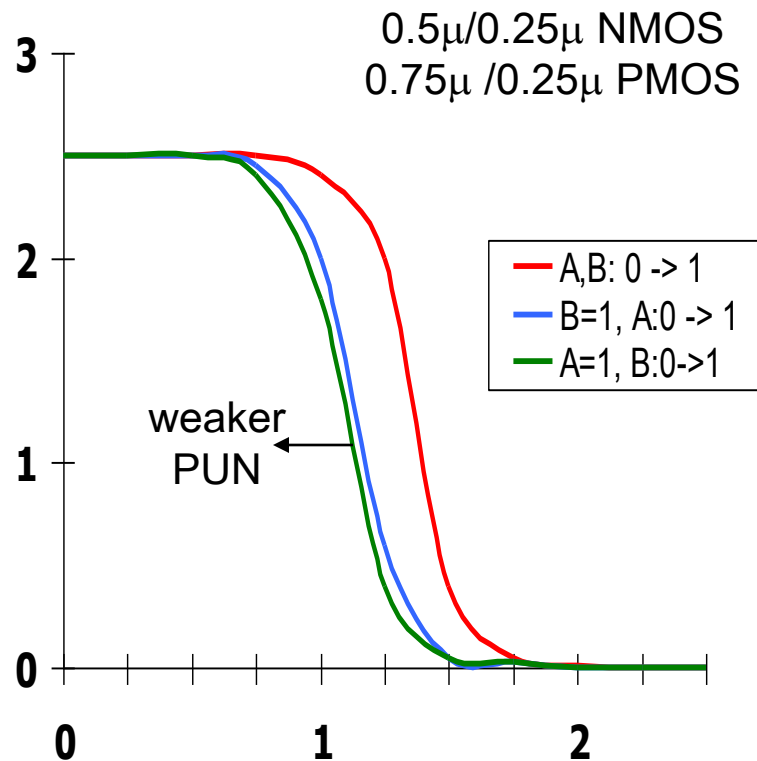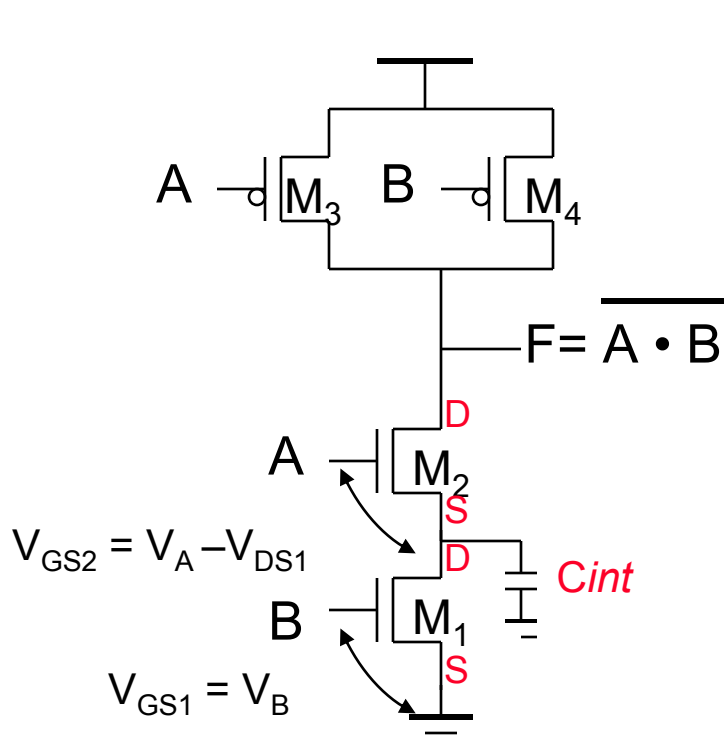

- The threshold voltage of M_2 is higher than M_1 due to the body effect (γ)


$$V_{Tn1} = V_{Tn0}$$

$$V_{Tn2} = V_{Tn0} + \gamma(\sqrt{(|2\phi_F| + V_{int})} - \sqrt{|2\phi_F|})$$

since V_{SB} of M_2 is not zero (when $V_B = 0$) due to the presence of C_{int}

Static CMOS Full Adder Circuit

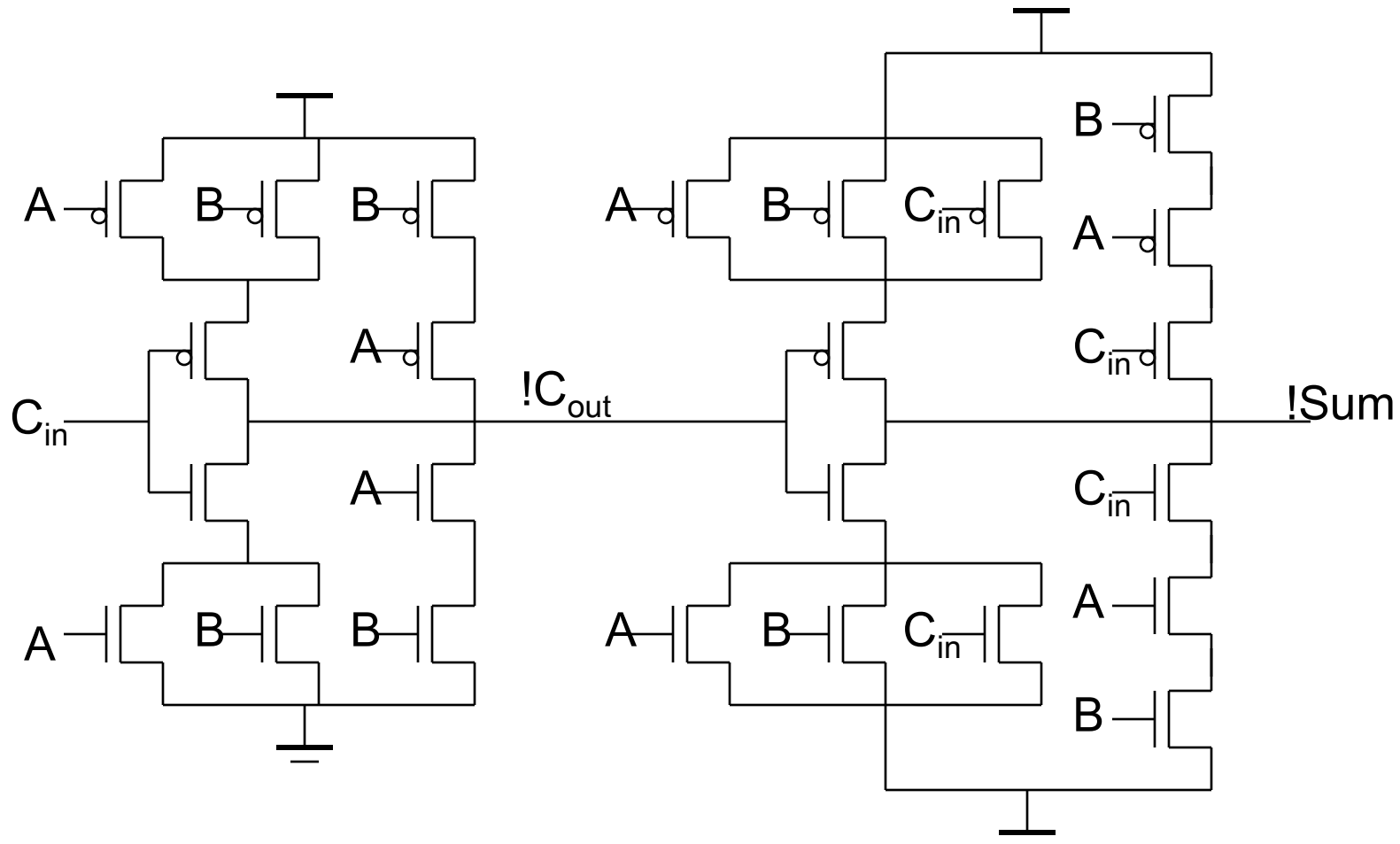
$$\neg C_{out} = \neg C_{in} \& (\neg A \mid \neg B) \mid (\neg A \& \neg B) \quad \neg Sum = C_{out} \& (\neg A \mid \neg B \mid \neg C_{in}) \mid (\neg A \& \neg B \& \neg C_{in})$$



$$C_{out} = C_{in} \& (A \mid B) \mid (A \& B)$$

$$Sum = \neg C_{out} \& (A \mid B \mid C_{in}) \mid (A \& B \& C_{in})$$

Next Time: Pass Transistor Circuits

 

Next Lecture and Reminders

□ Next lecture

- Pass transistor logic
 - Reading assignment – Rabaey, et al, 6.2.3

□ Reminders

- Project Title due today !
- Lecture 5 will be *next* Thursday (guest lecturer)
- HW2 due September 24th
- Evening midterm exam scheduled
 - Wednesday, October 10th from 8:15 to 10:15pm in 260 Willard
 - Only one midterm conflict filed for so far