

---

# **CSE477**

## **VLSI Digital Circuits**

### **Fall 2002**

## **Lecture 22: Shifters, Decoders, Muxes**

Mary Jane Irwin ( [www.cse.psu.edu/~mji](http://www.cse.psu.edu/~mji) )  
[www.cse.psu.edu/~cg477](http://www.cse.psu.edu/~cg477)

[Adapted from Rabaey's *Digital Integrated Circuits*, ©2002, J. Rabaey et al.]

# Review: Basic Building Blocks

---

## ❑ Datapath

### ❑ Execution units

- Adder, multiplier, divider, **shifter**, etc.

### ❑ Register file and pipeline registers

### ❑ **Multiplexers, decoders**

## ❑ Control

### ❑ Finite state machines (PLA, ROM, random logic)


## ❑ Interconnect

### ❑ Switches, arbiters, buses

## ❑ Memory

### ❑ Caches (SRAMs), TLBs, DRAMs, buffers


# Parallel Programmable Shifters

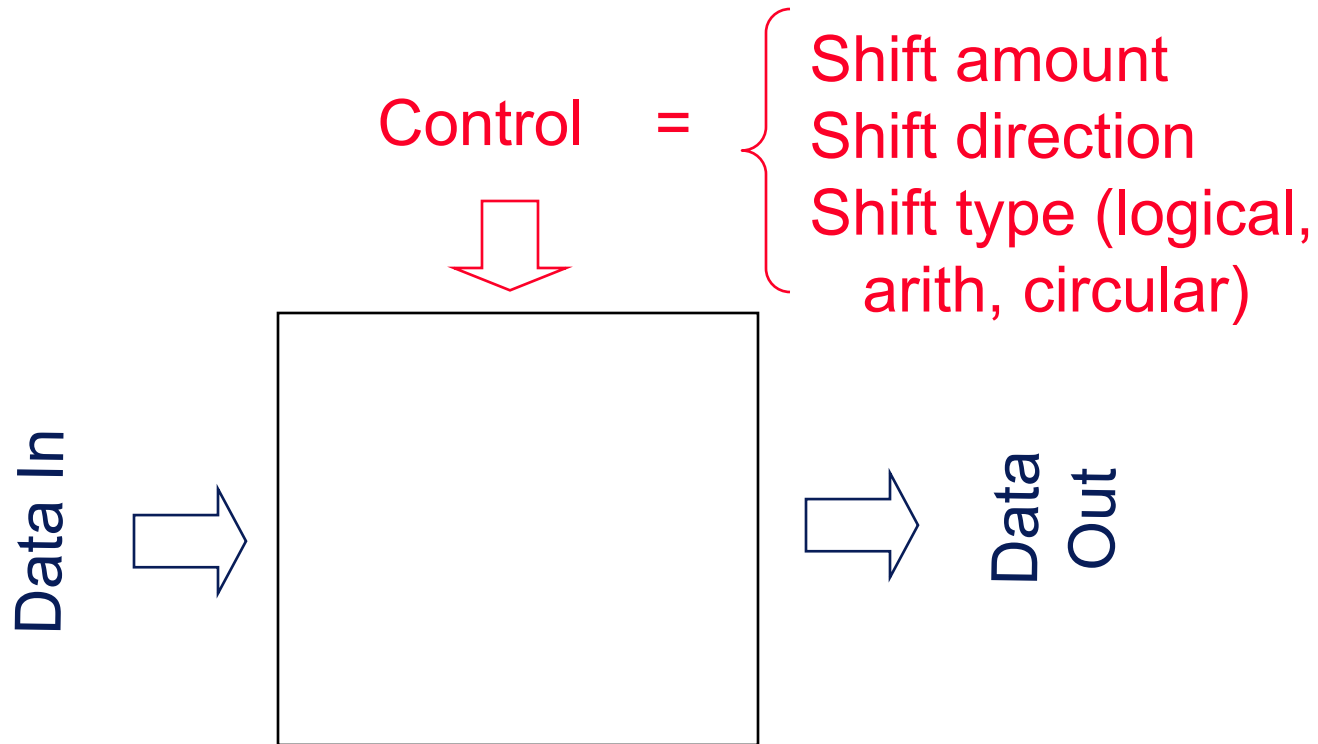

Shifters used in multipliers, floating point units


Consume lots of area if done in random logic gates

# A Programmable Binary Shifter

 

$A_i$	$A_{i-1}$	rgt	nop	left	$B_i$	$B_{i-1}$
$A_1$	$A_0$	0	1	0	$A_1$	$A_0$
$A_1$	$A_0$	1	0	0	0	$A_1$
$A_1$	$A_0$	0	0	1	$A_0$	0

# 4-bit Barrel Shifter

 

Example: **Sh0 = 1**

$$B_3B_2B_1B_0 = A_3A_2A_1A_0$$

**Sh1 = 1**

$$B_3B_2B_1B_0 = A_3A_3A_2A_1$$

**Sh2 = 1**


$$B_3B_2B_1B_0 = A_3A_3A_3A_2$$

**Sh3 = 1**

$$B_3B_2B_1B_0 = A_3A_3A_3A_3$$

Area dominated by wiring

# 4-bit Barrel Shifter Layout

 


Only one  $Sh\#$   
active at a time <sub>$i$</sub>

$$Width_{barrel} \sim 2 p_m N$$


$N$  = max shift distance,  $p_m$  = metal pitch

Delay  $\sim 1 f_{et} + N \text{ diff caps}$

# 8-bit Logarithmic Shifter

 

# 8-bit Logarithmic Shifter Layout Slice

 

$$\text{Width}_{\log} \sim p_m(2K + (1 + 2 + \dots + 2^{K-1})) = p_m(2^K + 2K - 1)$$

$$K = \log_2 N$$

$$\text{Delay} \sim K \text{ fets} + 2 \text{ diff caps}$$




# Shifter Implementation Comparisons

N	K	Barrel		Logarithmic	
		Width	Speed	Width	Speed
		$2 N p_m$	$1 + N \text{ diffs}$	$p_m(2^K + 2K - 1)$	$K + 2 \text{ diffs}$
8	3	$16 p_m$	$1 + 8$	$13 p_m$	$3 + 2$
16	4	$32 p_m$	$1 + 16$	$23 p_m$	$4 + 2$
32	5	$64 p_m$	$1 + 32$	$41 p_m$	$5 + 2$
64	6	$128 p_m$	$1 + 64$	$75 p_m$	$6 + 2$
 
# Decoders


---

- ❑ Decodes inputs to activate one of many outputs




- ❑ two inverters, four 2-input nand gates, four inverters plus enable logic
- ❑ how about for a 3-to-8, 4-to-16, etc. decoder?

# Dynamic NOR Decoder

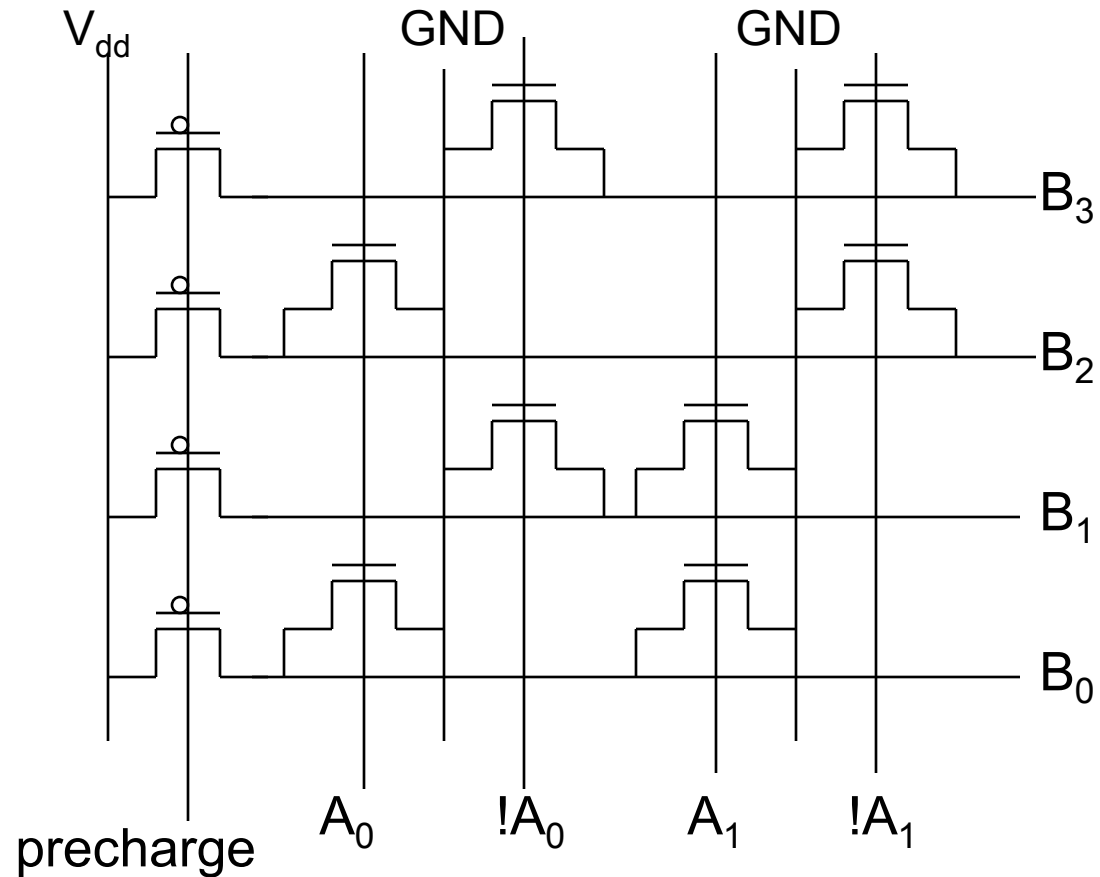


# Dynamic NAND Decoder

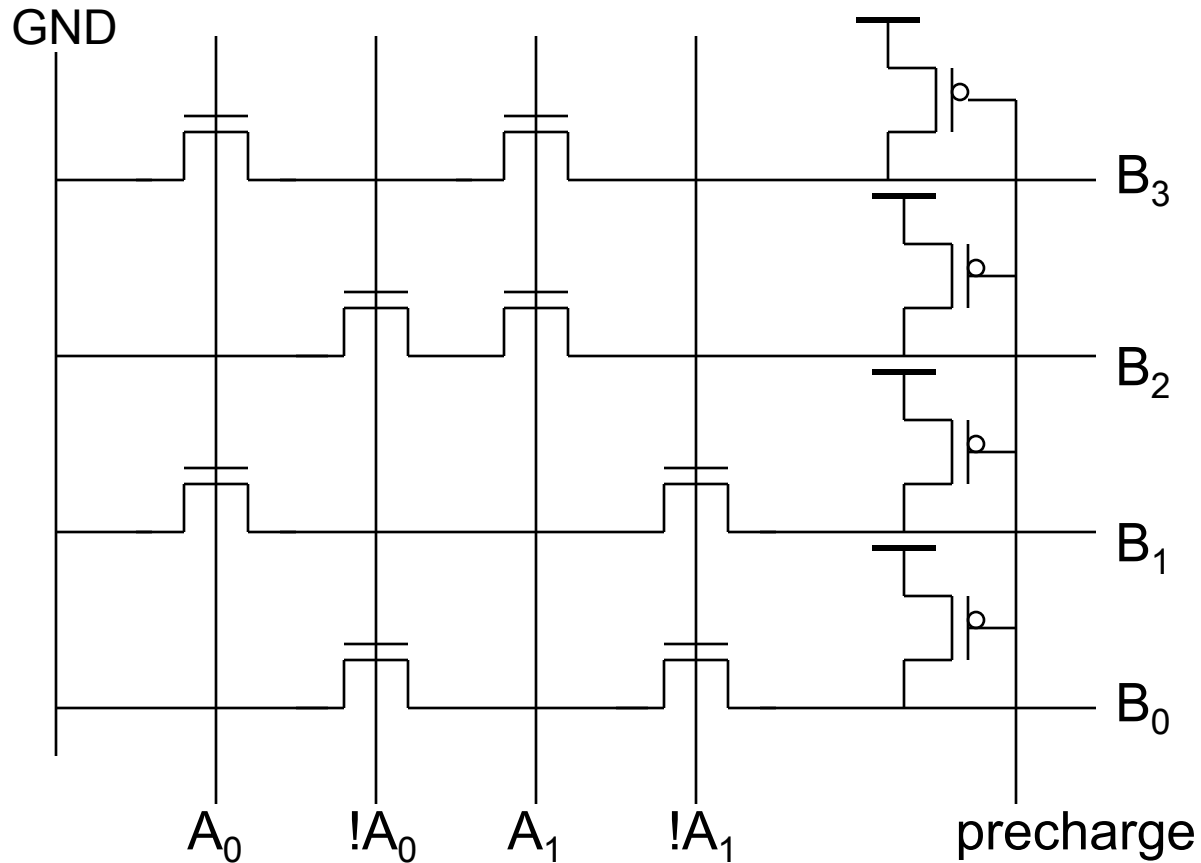


# Building Big Decoders from Small

Active low enable  
Active low output

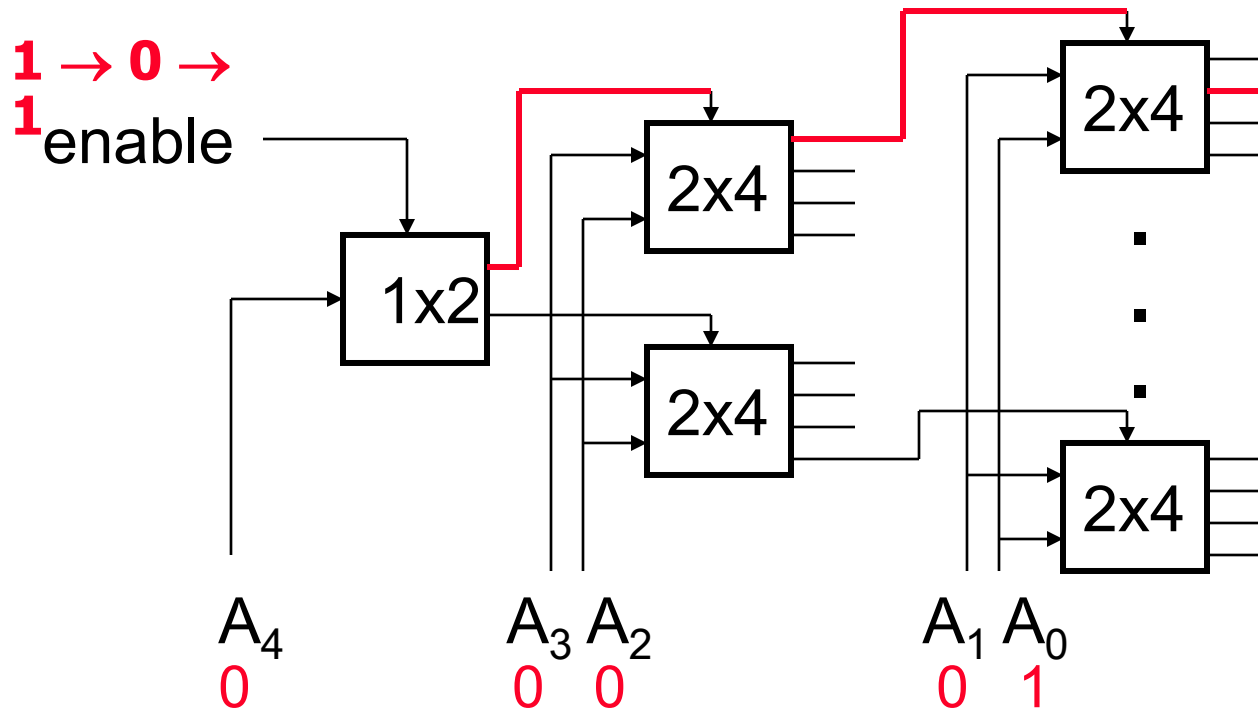

 
# Multiplexers

- ❑ Selects one of several inputs to gate to the single output




- ❑ two inverters, four 3-input nands, one 4-input nand
- ❑ how about for an 8x1, 16x1, etc. mux?

# Review: TG 2x1 Multiplexer

 


$$F = !((In_1 \& S) \mid (In_2 \& !S))$$

**GND**

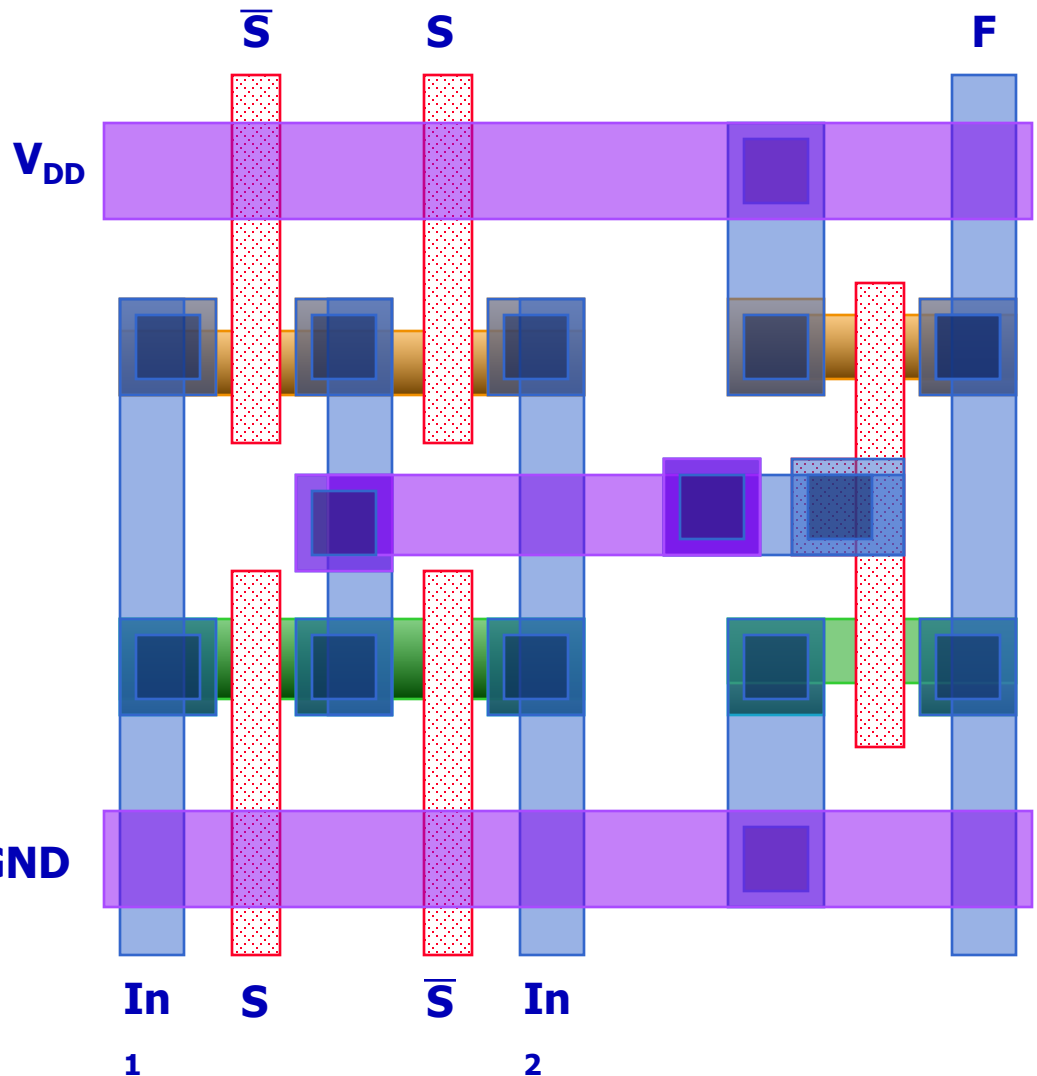


# Building Big Muxes from Small

 



 
# Review: Datapath Bit-Sliced Organization




Tile identical bit-slice elements

# Layout of Bit-Sliced Datapaths

 
 
# Layout of Bit-sliced Datapaths


**Without feedthroughs or  
pitch matching ( $4.2\mu\text{m}^2$ )**




**With feedthroughs  
( $3.2\mu\text{m}^2$ )**



 **With feedthroughs  
and pitch matching  
( $2.2\mu\text{m}^2$ )**



# Alpha 21264 Integer Unit Datapath

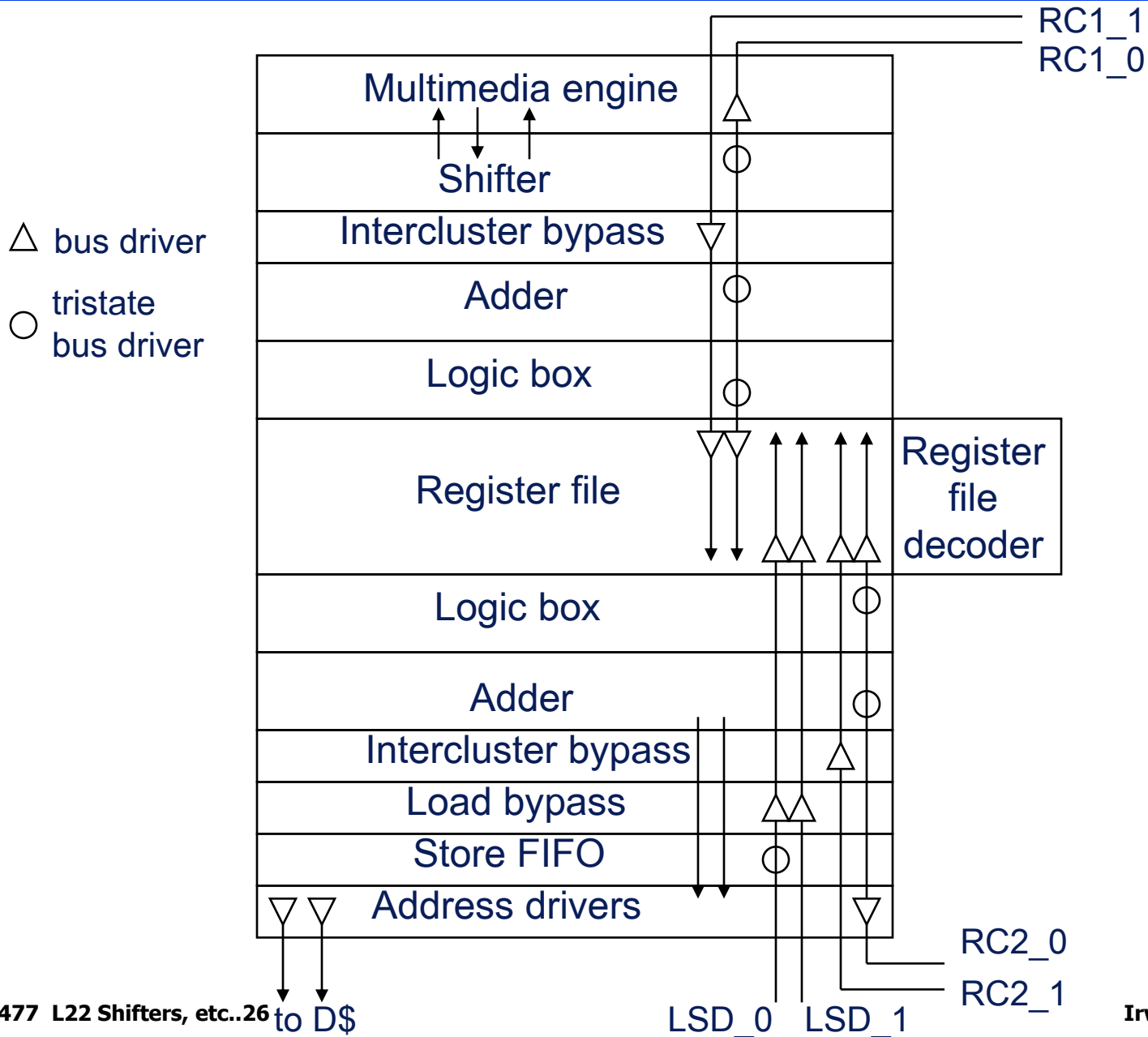

# Next Lecture and Reminders

---

## □ Next lecture

### □ Semiconductor memories

- Reading assignment – Rabaey, et al, 12.1-12.2.1

## □ Reminders

### □ Project final reports due December 5<sup>th</sup>

### □ HW5 (last one!) due November 19<sup>th</sup>

### □ Final grading negotiations/correction (except for the final exam) must be concluded by December 10<sup>th</sup>

### □ Final exam scheduled

- Monday, December 16<sup>th</sup> from 10:10 to noon in 118 and 121 Thomas